



# Parallel-Connected SiC MOSFETs – Essence, Challenges, and Solutions

**Helong Li and Shuang Zhao**

Hefei University of Technology

helong.li@hfut.edu.cn, shuang.zhao@hfut.edu.cn

## Speakers' Biographies

---



**Helong Li** is currently a Professor at Hefei University of Technology. He received B.Sc. and M.Sc. degree in Electrical Engineering from Harbin Institute of Technology, in 2010 and 2012, respectively, and received the Ph.D. degree from Aalborg University, Denmark, in 2015. From 2016 to 2019, he worked at Dynex Semiconductor Ltd, as Senior and Principal R&D Engineer, for power semiconductor packaging, testing, reliability. From 2019 to 2021, he worked at CREE Europe GmbH in the field of SiC automotive applications. He supported mainstream automotive customers in Europe and has good insight on SiC power modules in automotive applications. Since 2021, he has been with Hefei University of Technology as a professor in power electronics, mainly focusing on power semiconductor packaging and applications. Dr. Li has received Hubing Scholar from Hefei University of Technology in 2022. He published more than 50 scientific papers. Dr. Li also participated in the definition of automotive standard AQG324 for SiC power modules.



**Shuang Zhao** is currently an Associate Professor at Hefei University of Technology. He receives BSEE and MSEE from Wuhan University, Wuhan, China in 2012 and 2015 respectively, and obtains his PhD degree from University of Arkansas, Fayetteville, AR, USA in 2019. He was an intern at ABB US Corporate Research Center, Raleigh, North Carolina in 2018. From 2019 to 2021, he was serving as a Product Application Engineer at Automotive Group, Infineon Technologies Americas Corp, El Segundo, California, USA. He has supported multiple Tier 1 suppliers and OEMs. In 2021, he returned to China and joined Hefei University of Technology. He is also serving as a senior researcher at Hefei Comprehensive National Scientific Center, Hefei, China. His research interests include wide bandgap devices modeling, gate driving and applications. He has published over 30 peer-review papers, holds 2 US patents and 6 pending China patents. He is serving as an editor and a reviewer for multiple journals and a session chair for ECCE and APEC. He is a recipient of 2018 IEEE APEC Outstanding Presentation Award. He is a member of IEEE PELS TC2, IAS PEDCC, Eta Kappa Nu and a Senior Member of China Electrotechnical Society

# About HFUT and the Team



**Hefei:** An Innovation Center of China



**HFUT:** Hefei University of Technology



**Hefei Comprehensive National Science Center**



## Packaging Lab

power semiconductor packaging:  
wire-bonding, soldering, Ag-  
sintering, Gel-filling, plasma-  
cleaning, etc.




## Reliability Lab

HTRB, HTGB, H3TRB, power  
cycling, thermal shock, salt mist,  
SAM, X-Ray, and other inspection  
tools.
 
### ➤ All about power semiconductor:

- Packaging
- Aging & Testing
- Gate Driving & Modeling
- Applications: ATV, PV, ESS, Grid...



# Seminar Schedule

- 40 mins **Parallel connection of SiC MOSFETs in Multichip Power Modules**
- 40 mins **Active current sharing methodologies**

# Part I - Parallel Connection of SiC MOSFETs

- **Status and Challenges of Paralleling SiC MOSFETs**
- **Current Distribution among Paralleled Devices**
  - Influence of device and circuit parameters mismatches
  - Paralleling dies and paralleling half bridges
  - Essence of current imbalance
- **Optimization of Multichip Power Module Layout**


# Part I - Parallel Connection of SiC MOSFETs

01

Status and Challenges




# SiC MOSFET vs Si IGBT

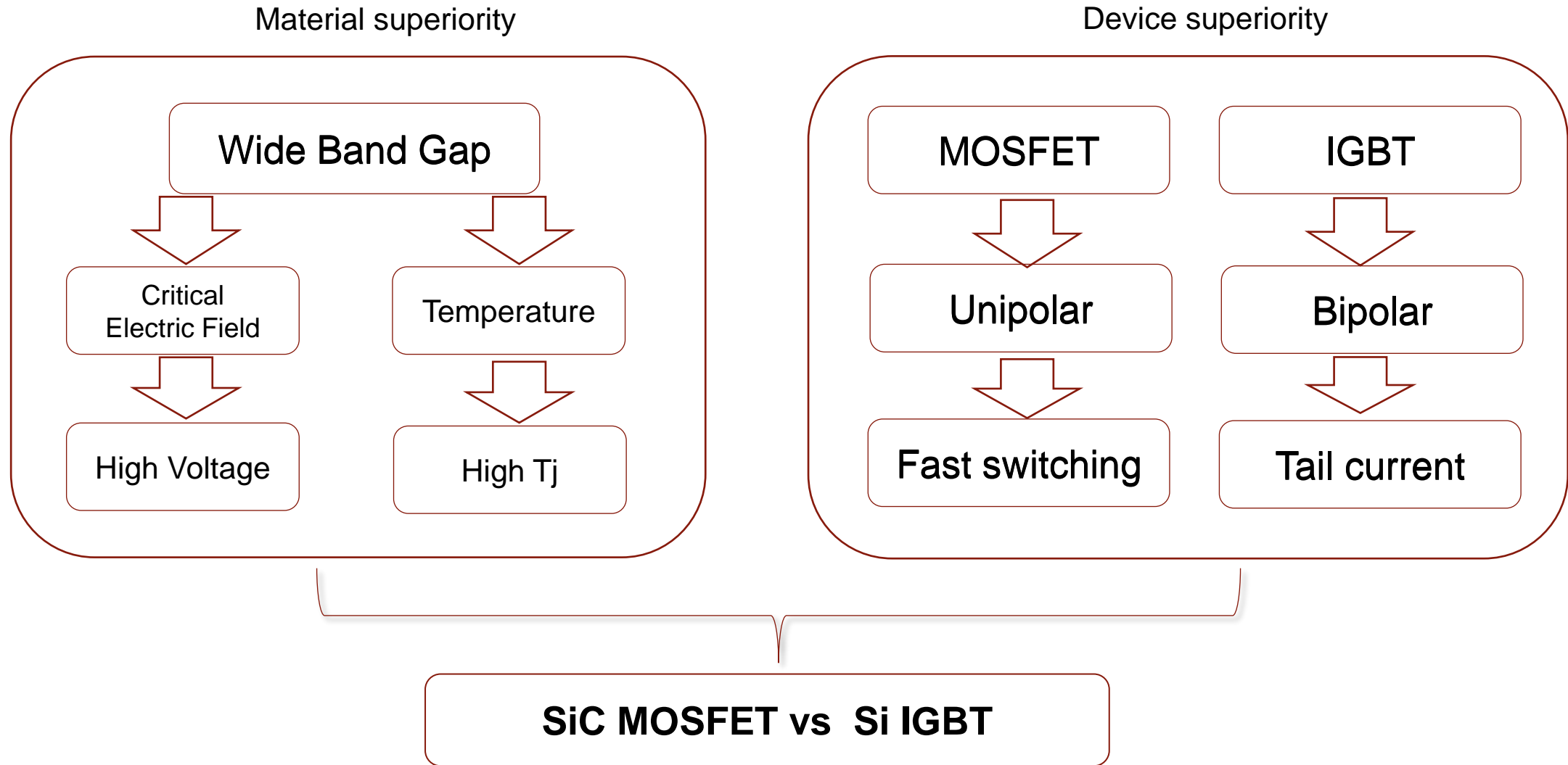


 
# Parallel Connection of Silicon Carbide MOSFETs




Parallel Unit Cells



Parallel Discrete Devices



Parallel Bare Dies


 


Parallel Power modules





# Device failures with paralleled chips

 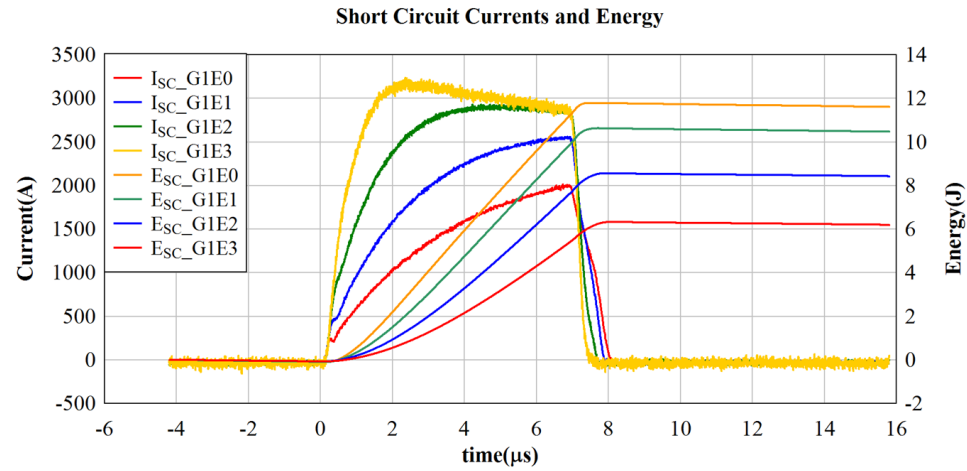

Over current and short circuit current device failures always at the same position



# Challenges of Paralleling SiC MOSFETs

## Si-IGBT

- 0 defect
- High mature process
- 8 or 12 inch
- >99% yield
- Large chip size




Si IGBT chip  
750V  
250A-300A

  


## SiC-MOSFET

- Material defect density
- Less mature process
- 4 or 6 inch
- Low yield
- Small chip size

SiC MOSFET chip  
750V  
80A-120A

 


# Challenges of Paralleling SiC MOSFETs

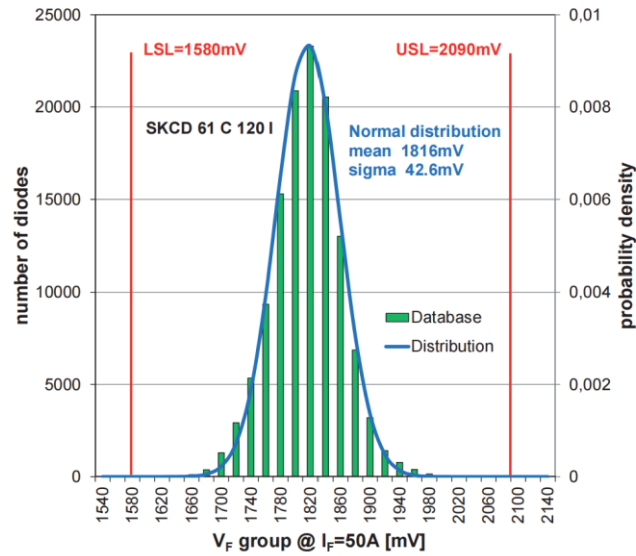

Device Parameter Distribution

Si Devices

Narrow and normal distribution

 


Device Parameter Distribution


SiC Devices

Wide and “wired” distribution



# Challenges of Paralleling SiC MOSFETs

 

3 x Si IGBT

 

8 x SiC MOSFETs

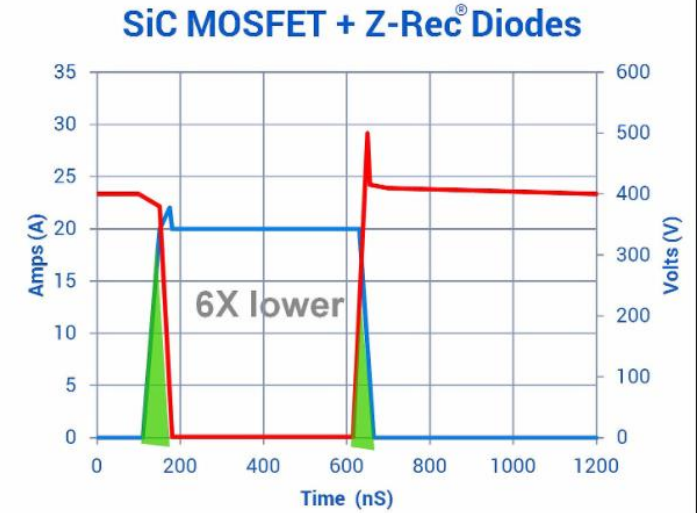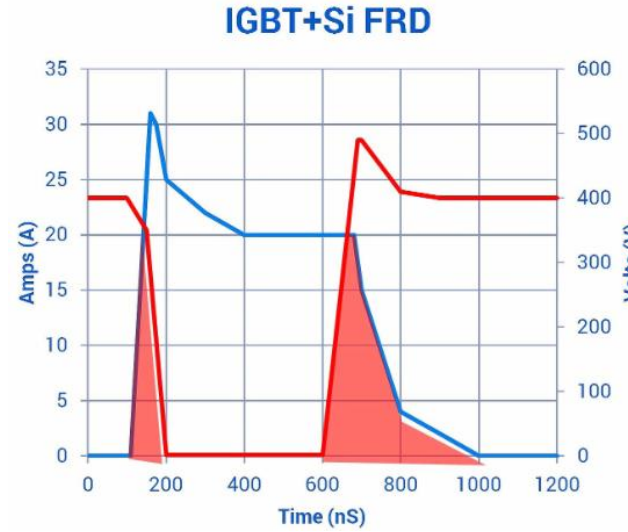


More chips to parallel


Faster switching speed
 
# Positive temperature coefficient

$$R_{dson} = R_{ch} + R_{drift} + R_{contact} + R_{sub}$$



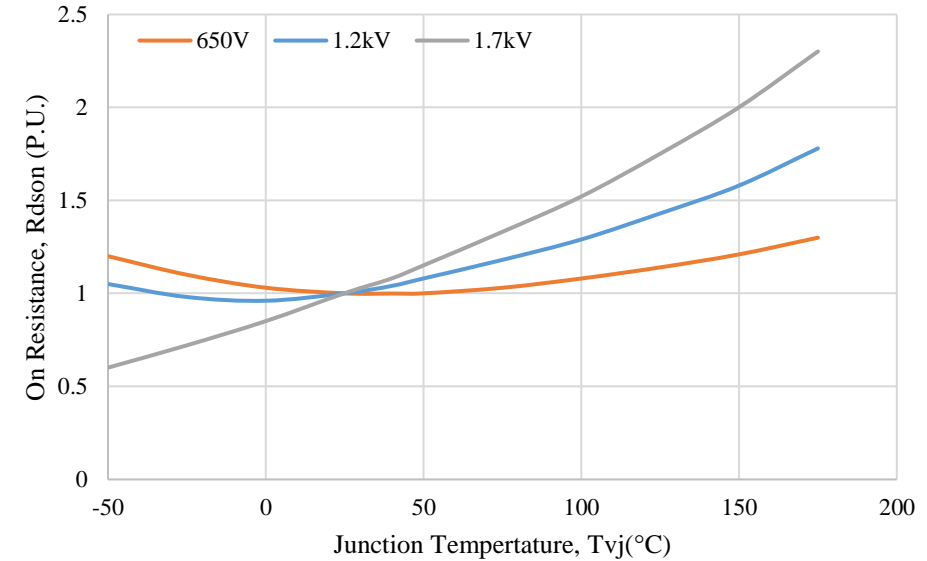Self-Balancing due to positive temperature coefficient



## Design Trade-off

Ration of ( $R_{dson}$  vs  $T_j$ )

- Higher ratio means more loss but easy for parallel connection
- Lower ratio means less loss but difficult for parallel connection

Higher voltage device has higher ratio of ( $R_{dson}$  vs  $T_j$ )

Due to:

- $R_{drift}$  have positive temperature coefficient
- $R_{ch}$  have negative temperature coefficient

# Part I - Parallel Connection of SiC MOSFETs



02

Current Distribution


 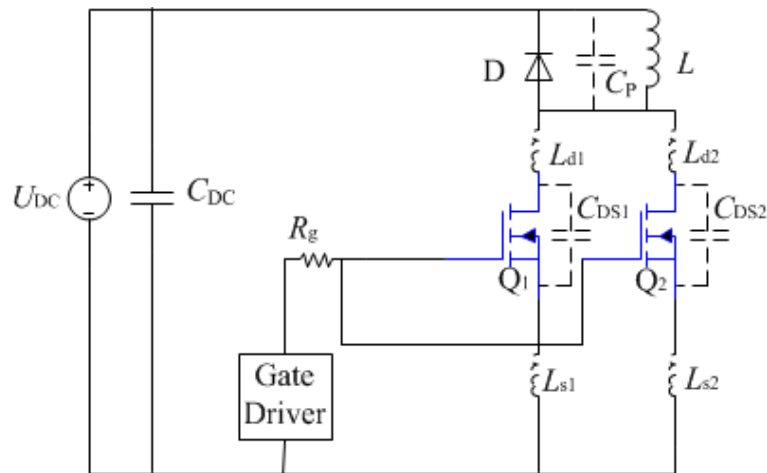
# Mechanism of Current Imbalance


- Device parameters mismatch
  - Influence of  $R_{on}$  mismatch
  - Influence of  $V_{th}$  mismatch
- Circuit parameters mismatch
  - Influence of  $L_d$  mismatch
  - Influence of  $L_s$  mismatch




- Symmetric layout design
- Easy to adjust circuit mismatch
- Good for benchmarking






# Current distribution

 

Devices output characterization

 





Devices transfer characterization

   






## Benchmarking

Current distribution without device parameters' mismatch and without circuit parameters' mismatch
    
# Current distribution with $L_d$ mismatch



     
# Current distribution with $L_s$ mismatch




- $L_s$  mismatch leads to transient current imbalance.
- Larger  $L_s$  leads to a smaller device turn-on current and smaller turn-on loss, while it leads to a slower turn-off current and larger turn-off loss.
- For parallel connection, larger  $L_s$  cause smaller device power losses. This is different with the effect of  $L_s$  for a single device.

# Multichip power modules layout


 


Customized 1.7kV/200A power module

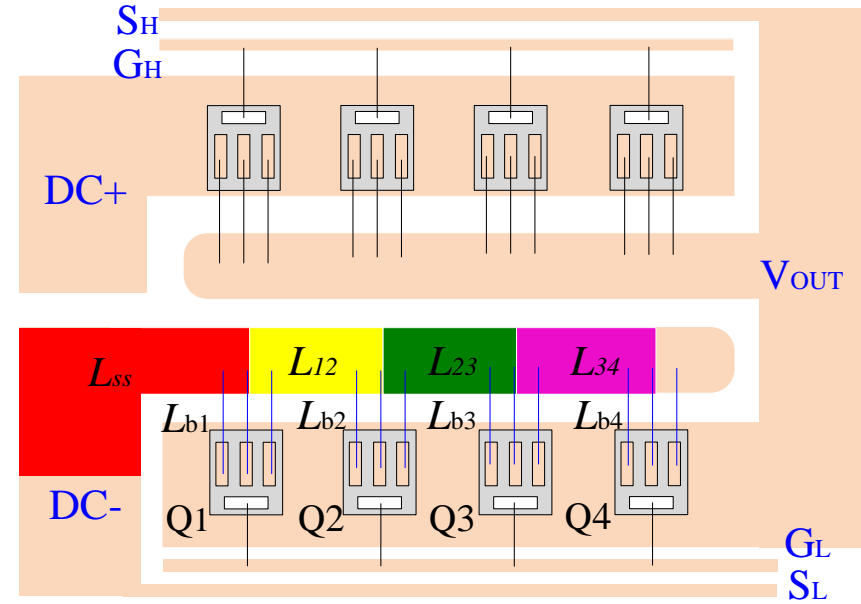



Power module layout
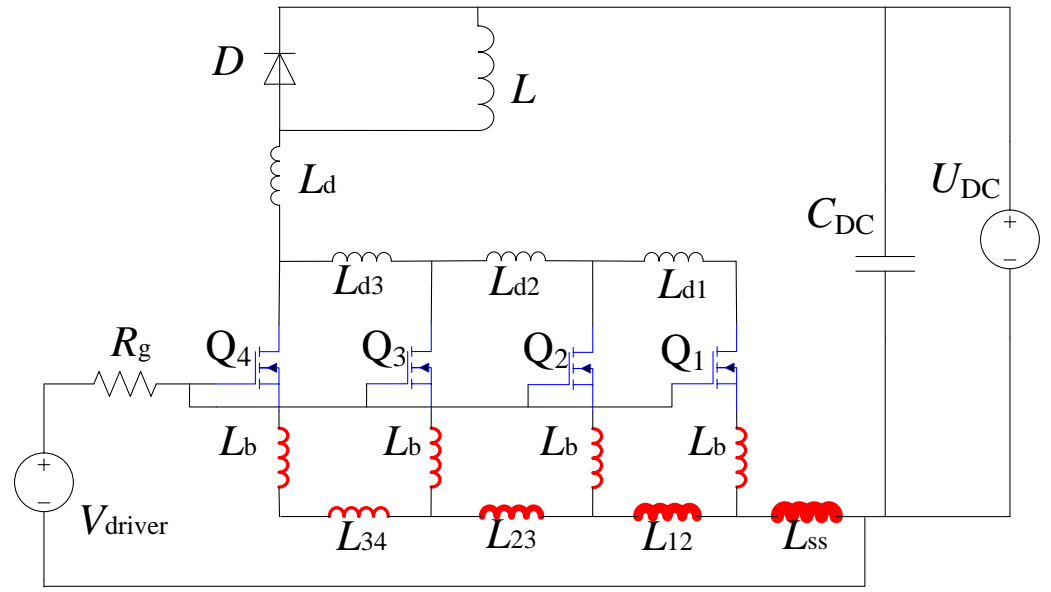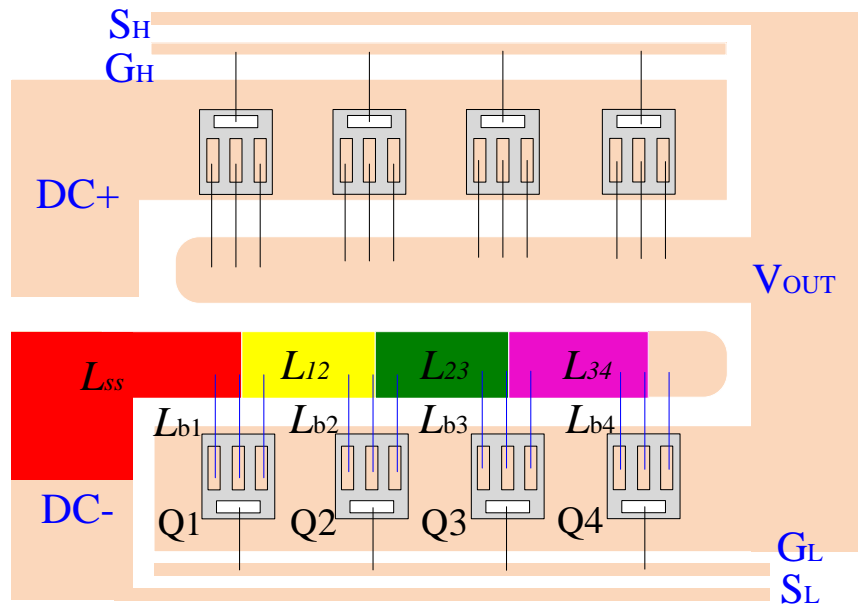
# Modeling of multichip power modules layout



Mismatch of  $L_s$

# Current coupling effects

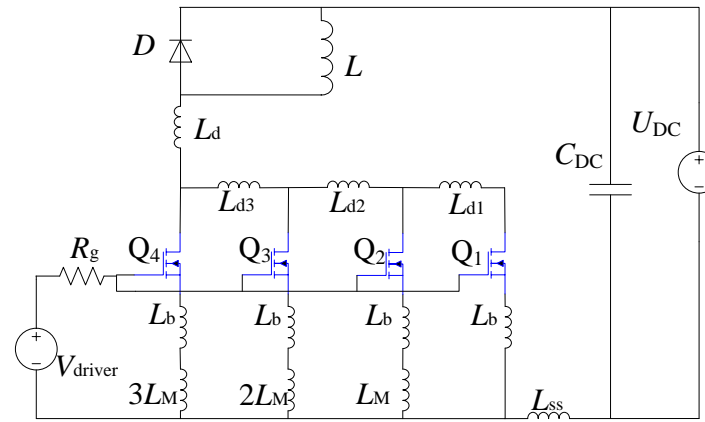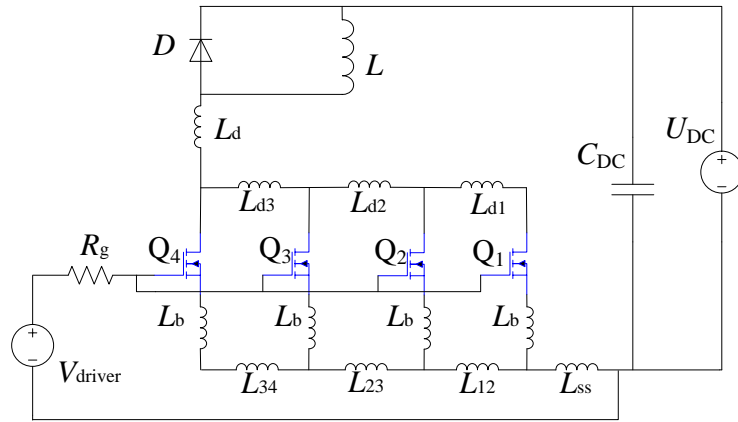

$$\begin{cases} L_{s1} = L_{ss} + L_b \\ L_{s2} = L_{ss} + L_{12} + L_b = L_{ss} + L_M + L_b \\ L_{s3} = L_{ss} + L_{12} + L_{23} + L_b = L_{ss} + 2L_M + L_b \\ L_{s4} = L_{ss} + L_{12} + L_{23} + L_{34} + L_b = L_{ss} + 3L_M + L_b \end{cases}$$

$$L \frac{di}{dt}$$

Identical mismatch value of  $L_s$

Difference

## Current Coupling Effect:



- The current on the mismatched  $L_s$  is not only from one device.
- The current of one device is not only affected by its own current but also the paralleled other devices.
- It is the mismatched  $L_s \cdot di/dt$  which affects VGS and therefore affects the transient current distribution.

# Current coupling effects

$$\begin{cases} i_{D1} - i_{D2} = g_{fs} (\Delta V_{LS2} - \Delta V_{LS1}) = g_{fs} \left[ L_b \frac{d(i_{D2} - i_{D1})}{dt} + L_{12} \frac{di_{D2}}{dt} \right] \\ i_{D2} - i_{D3} = g_{fs} (\Delta V_{LS3} - \Delta V_{LS2}) = g_{fs} \left[ L_b \frac{d(i_{D3} - i_{D2})}{dt} + L_{23} \frac{di_{D3}}{dt} \right] \\ i_{D3} - i_{D4} = g_{fs} (\Delta V_{LS4} - \Delta V_{LS3}) = g_{fs} \left[ L_b \frac{d(i_{D4} - i_{D3})}{dt} + L_{34} \frac{di_{D4}}{dt} \right] \\ i_{D1} - i_{D4} = g_{fs} (\Delta V_{LS4} - \Delta V_{LS1}) = g_{fs} \left[ L_b \frac{d(i_{D4} - i_{D1})}{dt} + (L_{12} + L_{23} + L_{34}) \frac{di_{D4}}{dt} \right] \end{cases}$$


$$\begin{cases} i_{D1} - i_{D2} = g_{fs} (\Delta V_{LS2} - \Delta V_{LS1}) = g_{fs} \left[ L_b \frac{d(i_{D2} - i_{D1})}{dt} + L_{12} \frac{di_{D2}}{dt} + L_{12} \frac{d(i_{D3} + i_{D4})}{dt} \right] \\ i_{D2} - i_{D3} = g_{fs} (\Delta V_{LS3} - \Delta V_{LS2}) = g_{fs} \left[ L_b \frac{d(i_{D3} - i_{D2})}{dt} + L_{23} \frac{di_{D3}}{dt} + L_{23} \frac{di_{D4}}{dt} \right] \\ i_{D3} - i_{D4} = g_{fs} (\Delta V_{LS4} - \Delta V_{LS3}) = g_{fs} \left[ L_b \frac{d(i_{D4} - i_{D3})}{dt} + L_{34} \frac{di_{D4}}{dt} \right] \\ i_{D1} - i_{D4} = g_{fs} (\Delta V_{LS4} - \Delta V_{LS1}) = g_{fs} \left[ L_b \frac{d(i_{D4} - i_{D1})}{dt} + (L_{12} + L_{23} + L_{34}) \frac{di_{D4}}{dt} + L_{12} \frac{d(i_{D2} + i_{D3})}{dt} + L_{23} \frac{di_{D3}}{dt} \right] \end{cases}$$

**Current coupling effect**

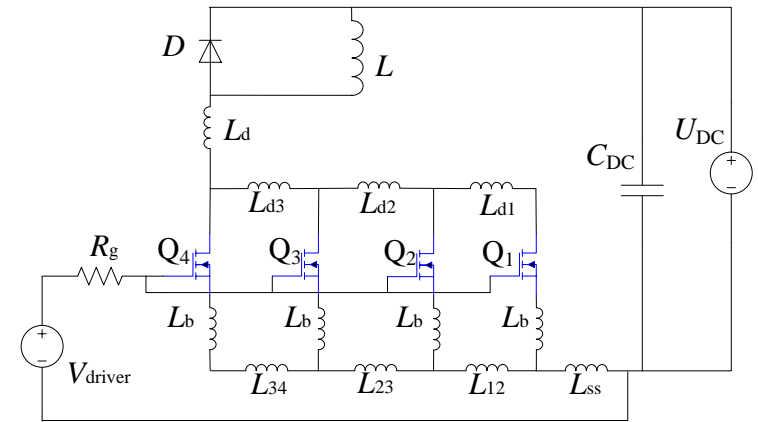
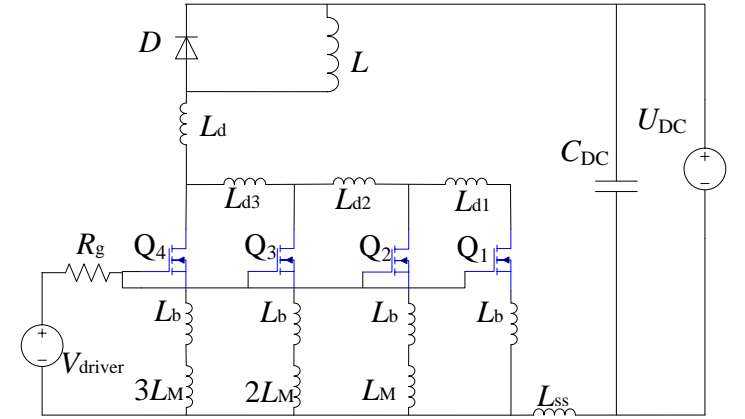





# Simulation results

 





With current coupling

  

Without current coupling



 


# Simulation and Experimental Comparison

    




H. Li, S. Munk-Nielsen, X. Wang, R. Maheshwari, S. Beczkowski, C. Uhrenfeldt, Toke Franke, 'Influences of device and circuit mismatches on paralleling silicon carbide MOSFETs', *IEEE Transaction on Power Electronics*, Volume 31, issue 1, 2016, Pages: 621 - 634.
 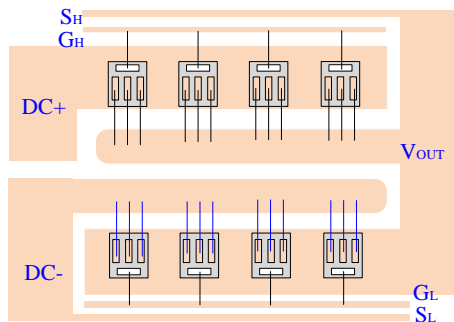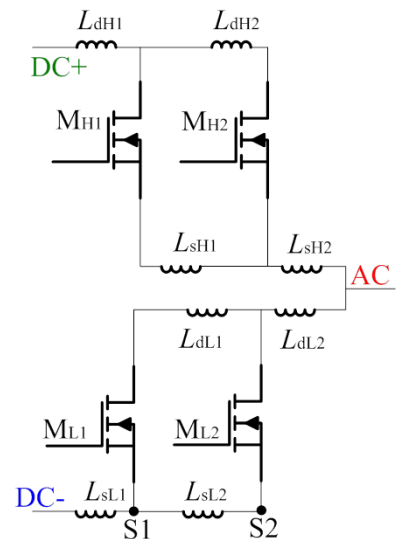
# Paralleling dies or Paralleling half bridges


 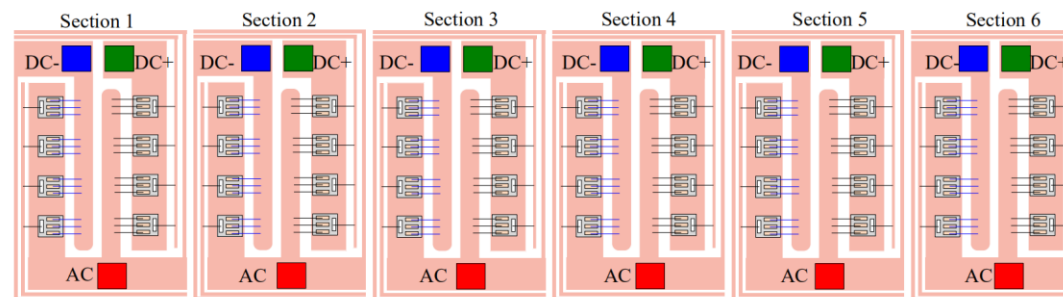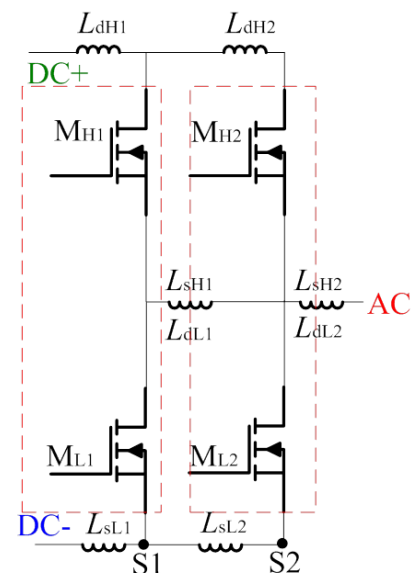
## Paralleling dies:





The devices are first paralleled to form a switch and then connected to form a half bridge.







## Paralleling half bridges:

The devices are connected both in parallel and in half bridge configuration. The key is that it can be split into separate half bridges.
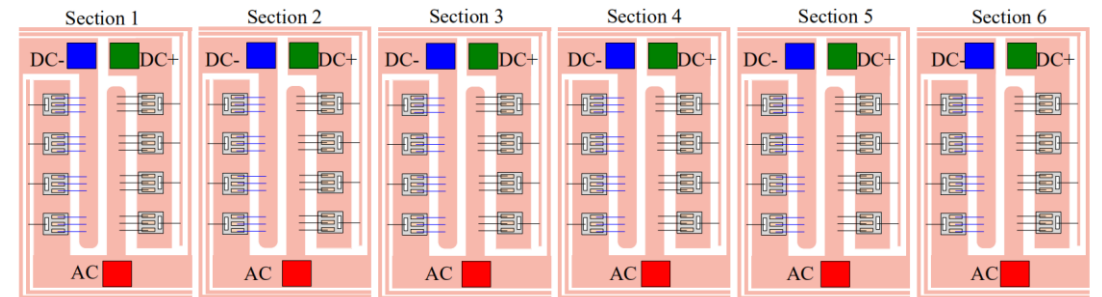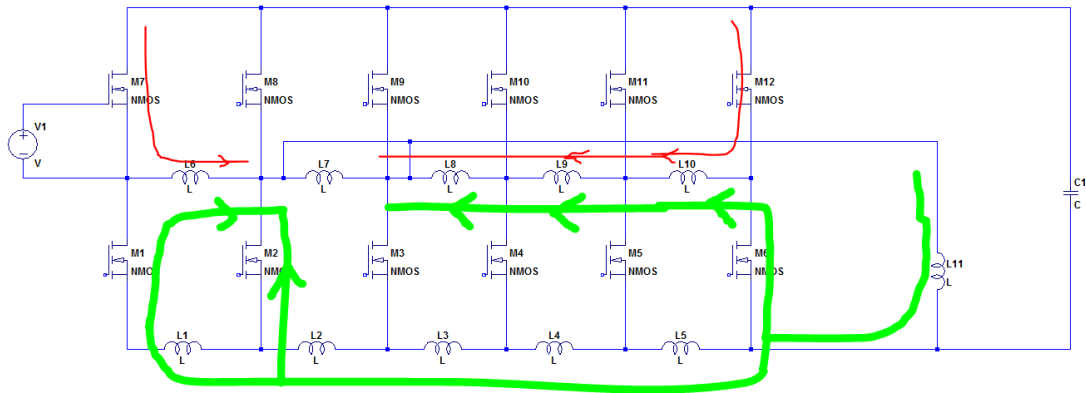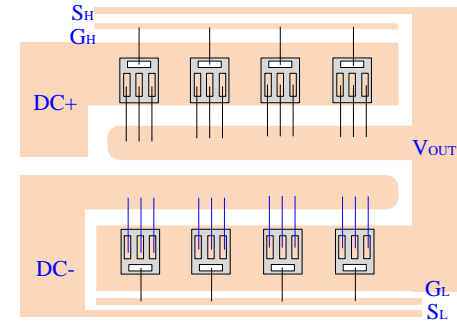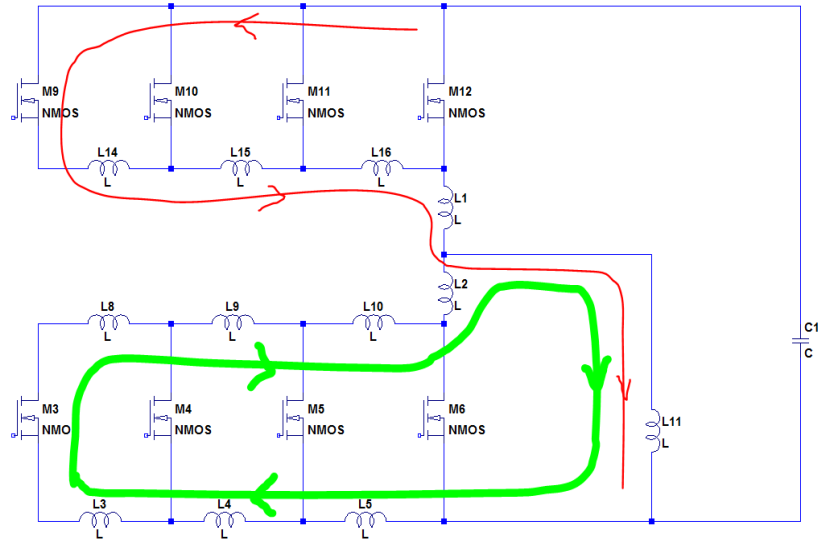
# Current commutation loop of paralleling dies







# Simulation Results

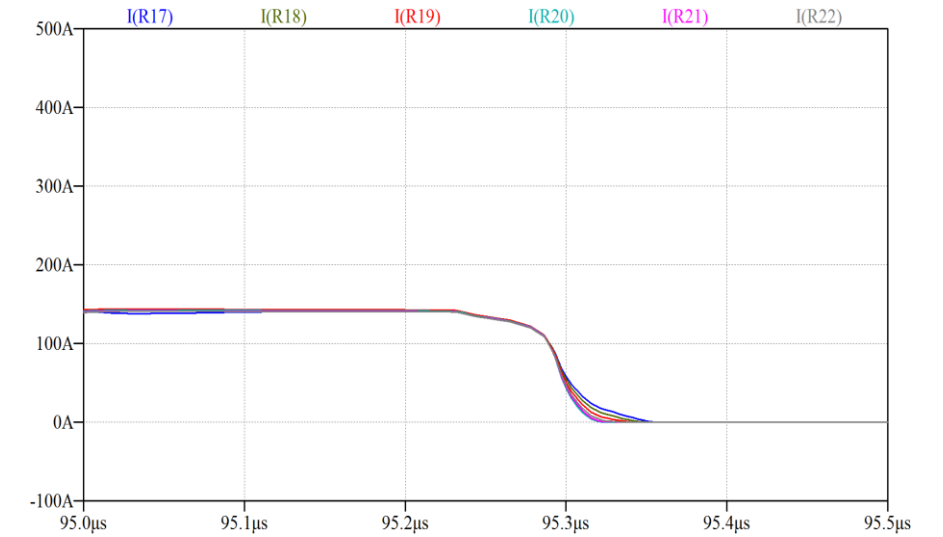   

Current distribution among low side substrates

Current distribution among high side substrates
  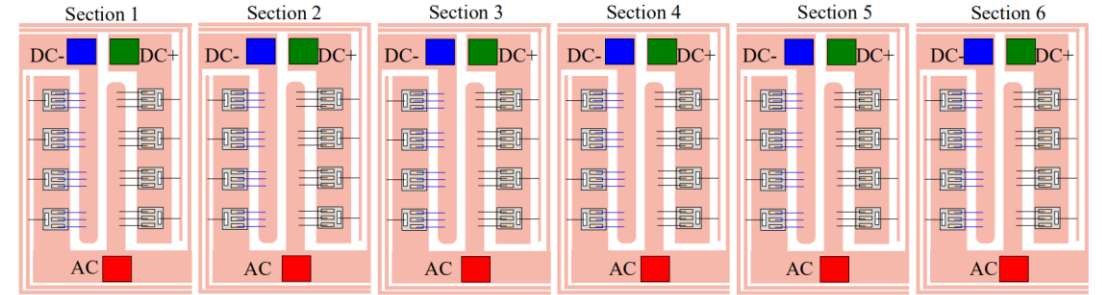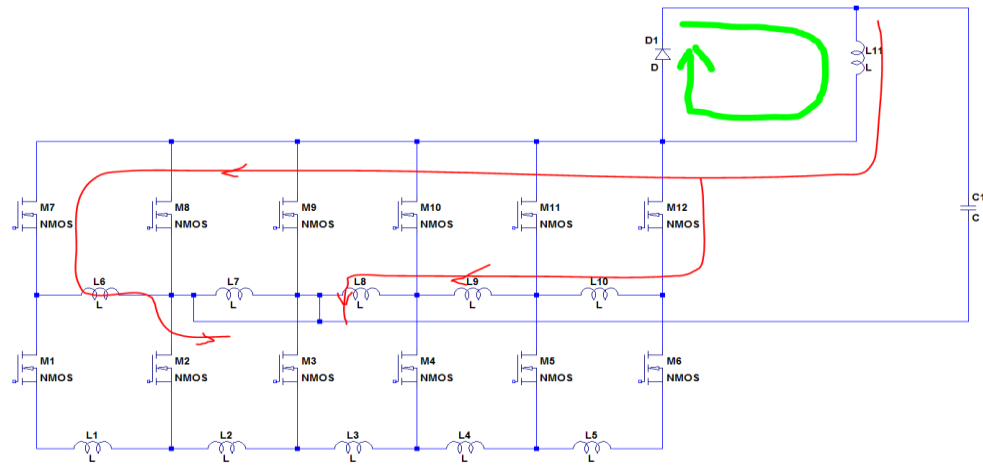
# Simulation of high side switch in another way



# Part I - Parallel Connection of SiC MOSFETs


03

● Optimization of package layout ●


---






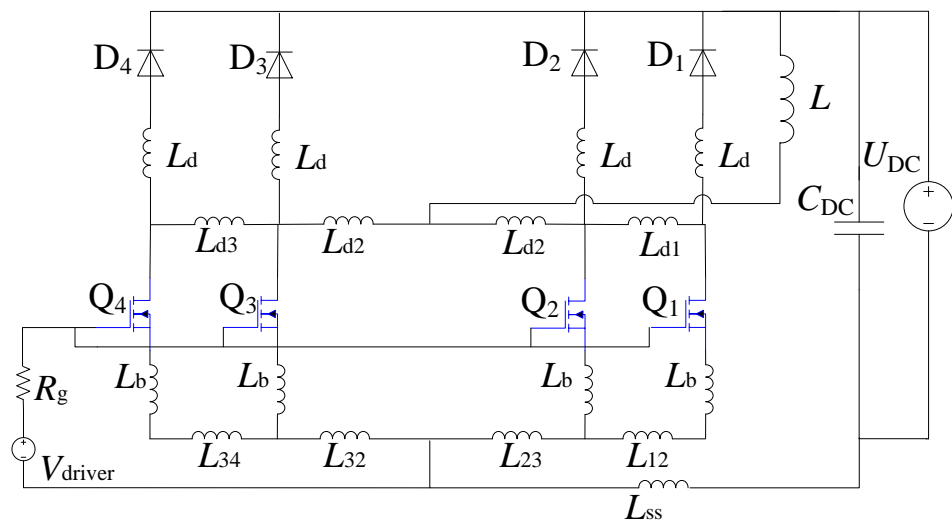
# Passive solution: Optimization of package layout


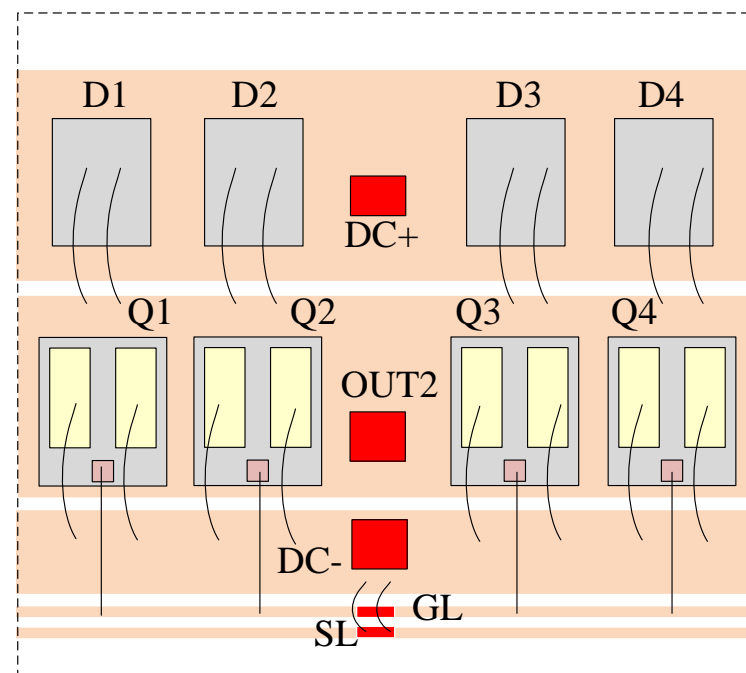
$$\begin{cases} i_{D2} - i_{D1} = g_{fs} \left[ L_b \frac{d(i_{D1} - i_{D2})}{dt} + L_{12} \frac{di_{D1}}{dt} \right] \\ i_{D2} - i_{D3} = 0 \\ i_{D3} - i_{D4} = g_{fs} \left[ L_b \frac{d(i_{D4} - i_{D3})}{dt} + L_{34} \frac{di_{D4}}{dt} \right] \\ i_{D1} - i_{D4} = 0 \end{cases}$$







# Experimental Results

   
 


H. Li, S. Munk-Nielsen, S. Beczkowski, X. Wang, 'A Novel DBC layout for current imbalance mitigation in SiC MOSFET multichip power module', IEEE Transaction on Power Electronics Letters, 2016


# Swap DC+ and DC- screw terminals

    

Slightly improved

 
 


# Modified bus bar structure




 

  
## Redesign busbar structure of the module

- Redirect the current flow
- Reduce  $L_s$  mismatch
- Reduce  $di/dt$  applied on mismatched  $L_s$



# Simulation Tool

 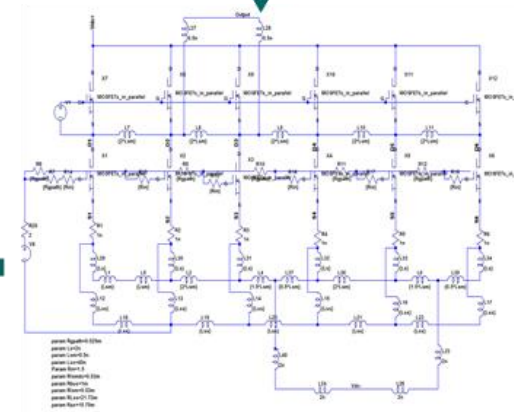  

No

Optimized?

New layout design

Next process

YES

- Current imbalance causes:

- Mismatch of common source stray inductance
- $di/dt$  applied on the mismatched  $L_s$

- Effective methods for current imbalance mitigation

- Reduce the mismatch of common source stray inductance
- Reduce the  $di/dt$  on the mismatched common source stray inductance
- The key is to reduce the voltage potential differences between paralleled MOSFET source pads

# Parallel Connection of SiC MOSFETs

**Thanks!**

helong.li@hfut.edu.cn



# Part II – Active Current Sharing Methodologies

- **Two types of current imbalance: Static and transient**
- **Active current sharing methodologies**
  - **Passives-based current sharing strategy**
  - **Driver-based current sharing strategy**
- **Conclusions and insight**

# Part II – Active Current Sharing Methodologies


01

• Two types of current imbalance •


---

# Two Types of Current Imbalance: Static and transient
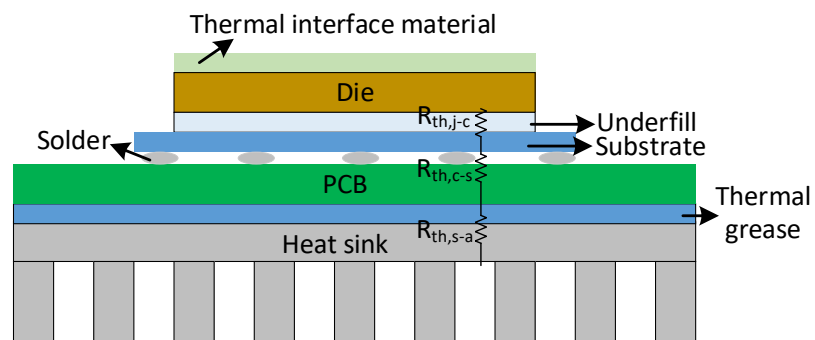
## Why does current sharing matter? – 1. Thermal issue



A typical structure of power device

 

The thermal network of the converter.

Power loss determines junction temperature!


### ➤ Two types of power loss

Conduction loss  $P_{cond} = I_{rms}^2 R_{ds,on}$

Switching loss  $P_{sw} = f_{sw} E_{sw} = \int V_{ds} I_{ds} dt$




Double pulse test setup

 



Switching loss characterization

# Two Types of Current Imbalance: Static and transient
 
## Why does current sharing matter? – 1. Thermal issue



  
1 Layer      2 Layer (L2-75um)      2 Layer (L2-150um)



The Flotherm simulation model of the device in DSO package

$$T_j = P_{loss} (R_{th,j-c} + R_{th,c-s} + R_{th,s-a}) + T_a$$
 
$$Z_{th(j-c)} = \frac{R_{th(j-c)}}{1 + j \cdot 2\pi f C_{th} \cdot R_{th}}$$




Top Side Cooled DSO



Bottom Side Cooled DSO



# Two Types of Current Imbalance: Static and transient
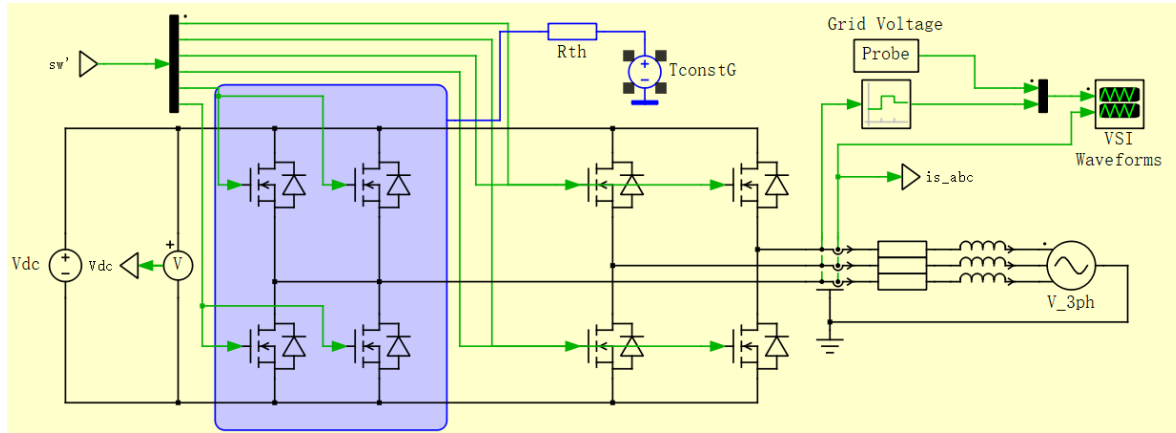
## Why current sharing matters? – 2. Reliability issue (lifetime)


  
### Coffin-Manson lifetime formula


$$N_f = A \cdot (\Delta T_j)^\alpha \cdot e^{E_a / (k_B \cdot T_m)}$$




The mismatching of  $I_{ds}$  can increase the  $T_{j,max}$  and raise long-term reliability concern

# Two Types of Current Imbalance: Static and transient
 
## Why does current sharing matter? – 2. Reliability issue (SOA)



 The worst case of current imbalance during turn-off transient




A typical safe operating area (SOA) of SiC MOSFET

### ❑ Catastrophic results:

Very high degree of imbalance -> Higher peak current -> Out of SOA

# Two Types of Current Imbalance: Static and transient

 
## Static imbalance: higher conduction loss




Trenchgate MOSFET

➤ ON-State resistance

 
$$\left\{ \begin{aligned} R_{ds1\_on} &= \frac{L}{W \mu_n C_{ox} (V_{gs1} - V_{th1})} \\ R_{ds2\_on} &= \frac{L}{W \mu_n C_{ox} (V_{gs2} - V_{th2})} \end{aligned} \right.$$



Equivalent circuit

 

 
I-V curve of 20 SiC MOSFETs with same part number




Static current imbalance

# Two Types of Current Imbalance: Static and transient

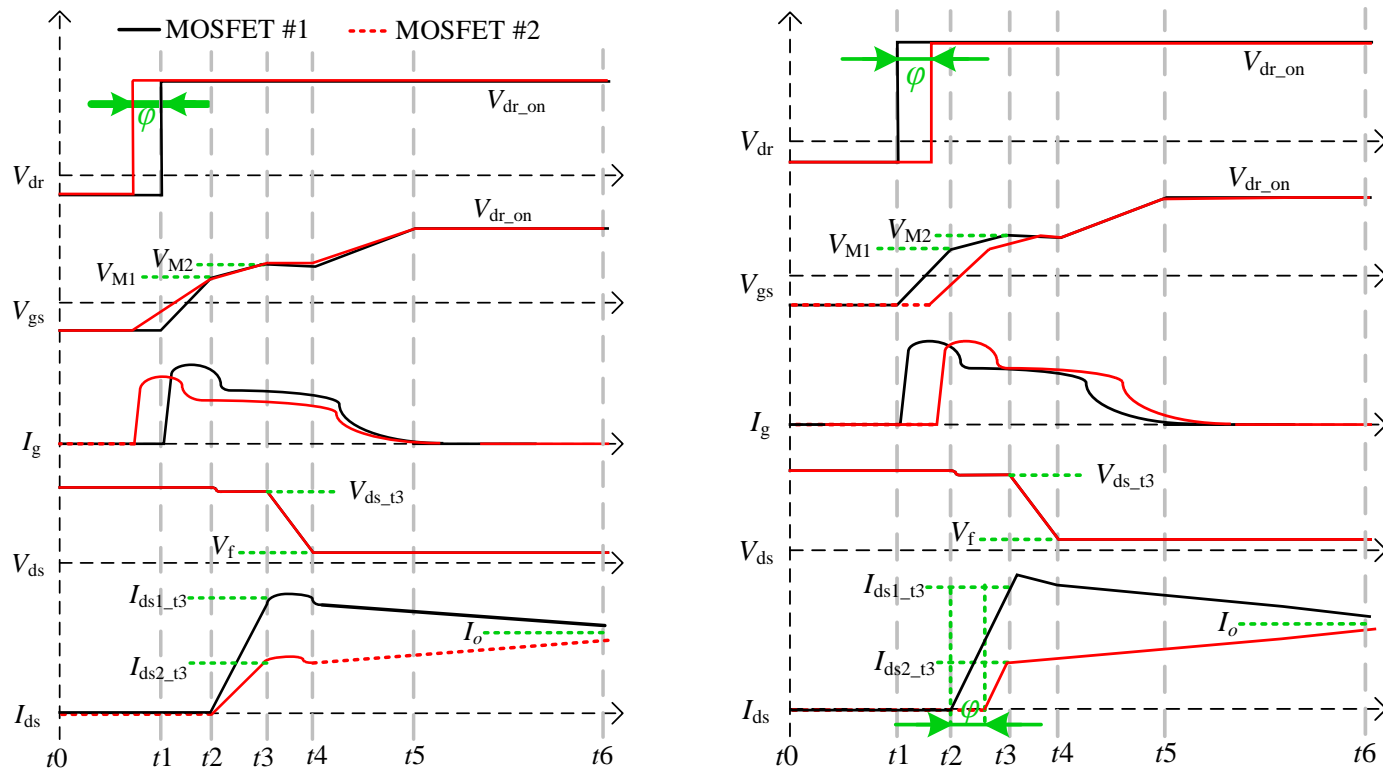
## Transient imbalance: higher peak current and switching loss



 Two simple modes of current imbalance:  
Different switching slew rate vs. Asynchronous gate signal



Turn-on transient imbalance

 


Turn-off transient imbalance




# Two Types of Current Imbalance: Static and transient

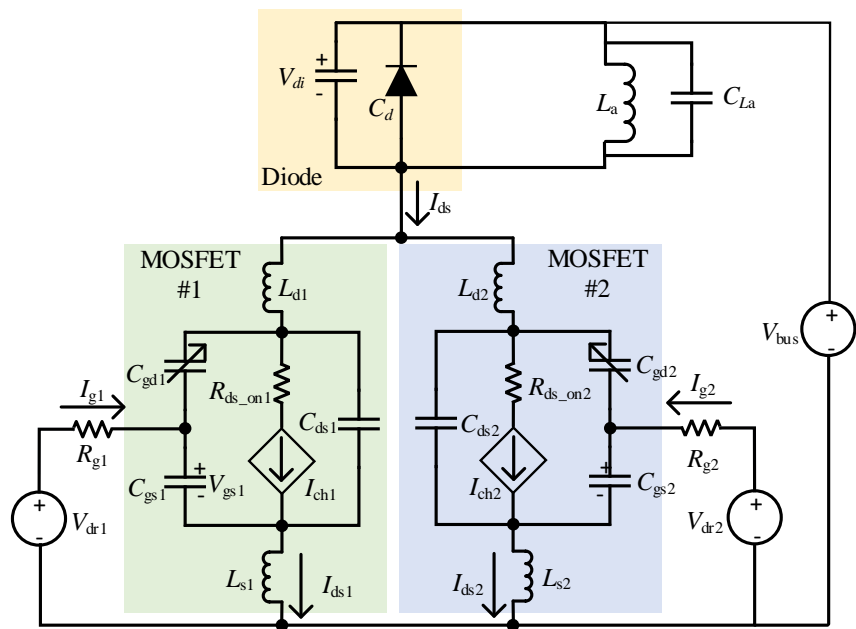
## What parameters impact the current distributions?



 Equivalent circuit of paralleling SiC MOSFETs



Inside the package

 

External circuit

Some parameters that affect the current balance on parallel-connected MOSFET

Category	Variable	Definition
Intrinsic parameters	$V_{th}$	Gate threshold voltage
	$C_{gd}$	Gate-drain capacitance
	$C_{gs}$	Gate-source capacitance
	$C_{ds}$	Drain-source capacitance
	$G_{fs}$	Transconductance
	$R_{ds\_on}$	On-state resistance
External parameters	$V_{dr}$	Driver voltage
	$L_d$	Drain inductance
	$L_s$	Source inductance
	$L_g$	Gate inductance
	$R_g$	Gate resistance
	$T_j$	Junction temperature
Status indicators	$V_{bus}$	Dc bus voltage
	$I_o$	Load current

# Part II – Active Current Sharing Methodologies



02

● Active current sharing methodologies ●


# Active Current Sharing Methodologies
 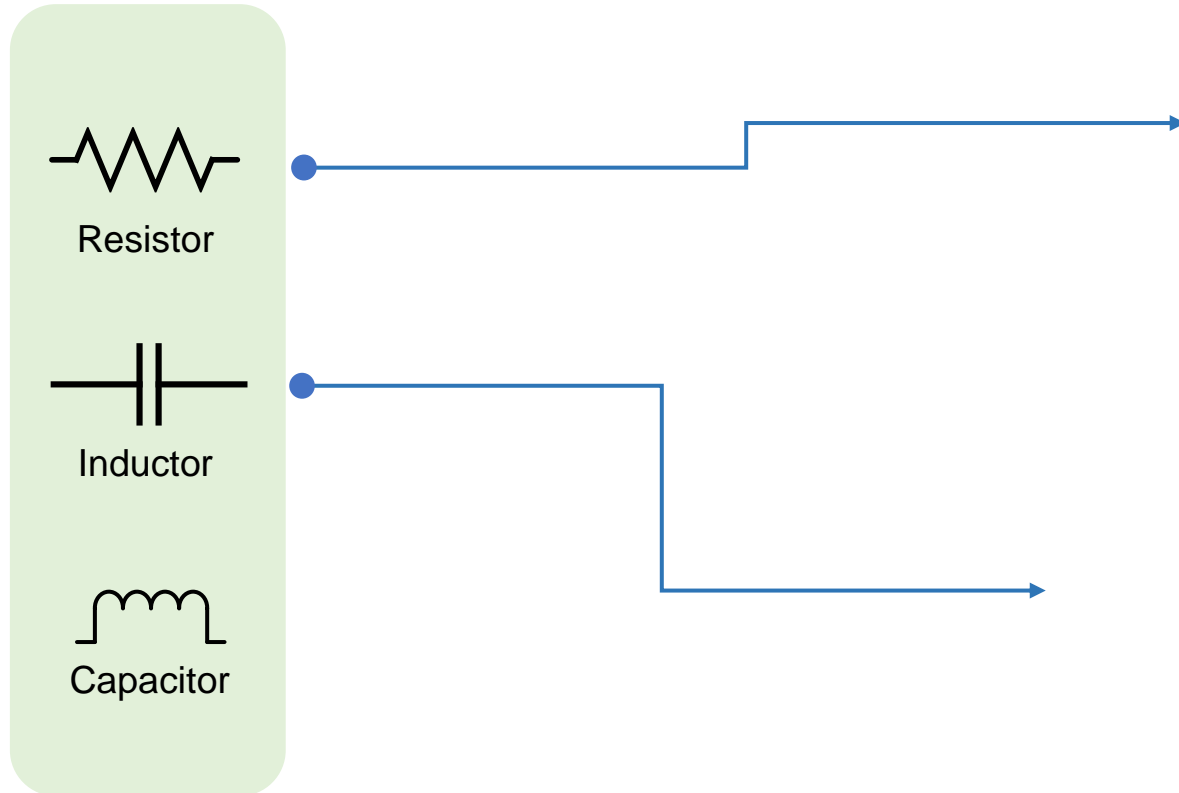
## What SOTA current sharing strategies do we have?

Passives-based sharing methodologies: employing external passive component to adjust the electrical parameters of the circuit




 
External series resistor: For static imbalance




External magnetics: For transient imbalance

- [1] L. Wang et al., "Cu clip-bonding method with optimized source inductance for current balancing in multichip SiC MOSFET power module," IEEE Trans. Power Electron., vol. 37, no. 7, Jul. 2022.
- [2] H. Wang, F. Wang, Power MOSFETs paralleling operation for high power high density converters, in Proc. IEEE IAS Annual Meeting Industry Applications Conference. Tampa, FL, USA, 2006.
- [3] Z. Zeng et al., "Imbalance current analysis and its suppression methodology for parallel SiC MOSFETs with aid of a differential mode choke," IEEE Trans. Ind. Electron., vol. 67, no. 2, 2020.

# Active Current Sharing Methodologies

 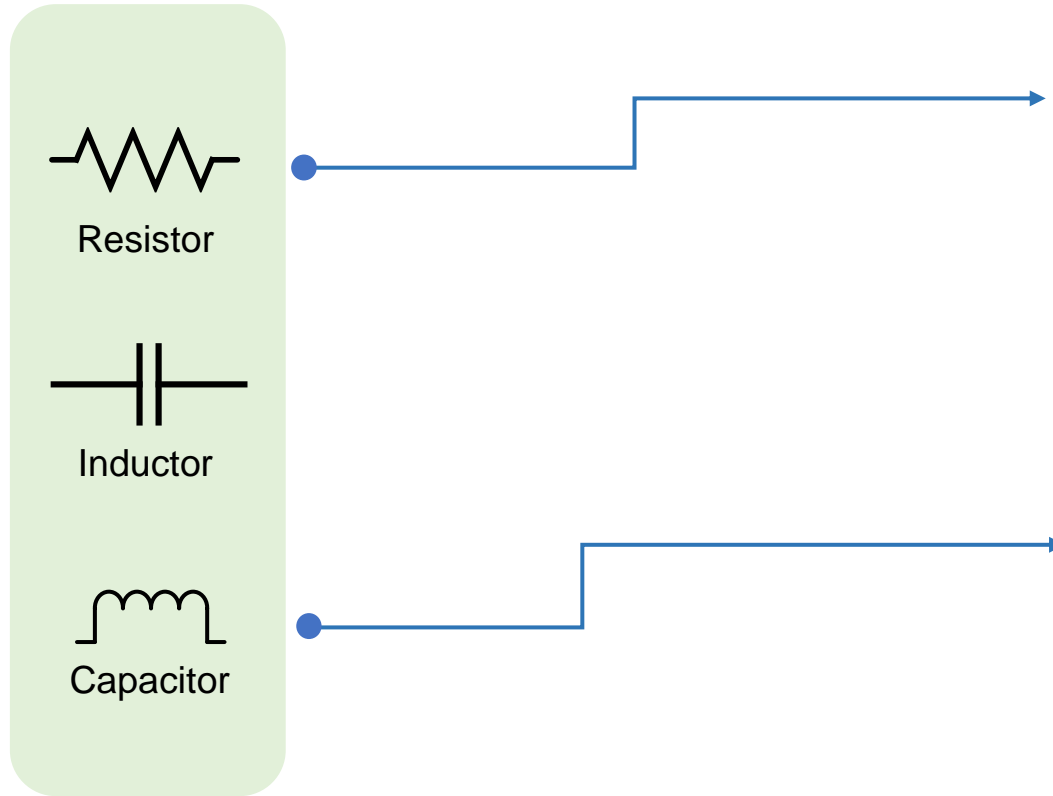

Hybrid passives: RLL network

 


External parallel capacitors: For transient imbalance on HB

- [1] J. Qu, Q. Zhang, X. Yuan and S. Cui, "Design of a paralleled SiC MOSFET half-bridge unit with distributed arrangement of DC capacitors," IEEE Trans. Power Electron., vol. 35, no. 10, pp. 10879-10891, Oct. 2020. .
- [2] Y. Wang, J. Wang, F. Liu, Q. Liu and R. Zou, "An RLL current sharing snubber for multiple parallel IGBTs in high power applications," IEEE Trans. Power Electron., vol. 37, no. 7, pp. 7555-7561, Jul. 2022.
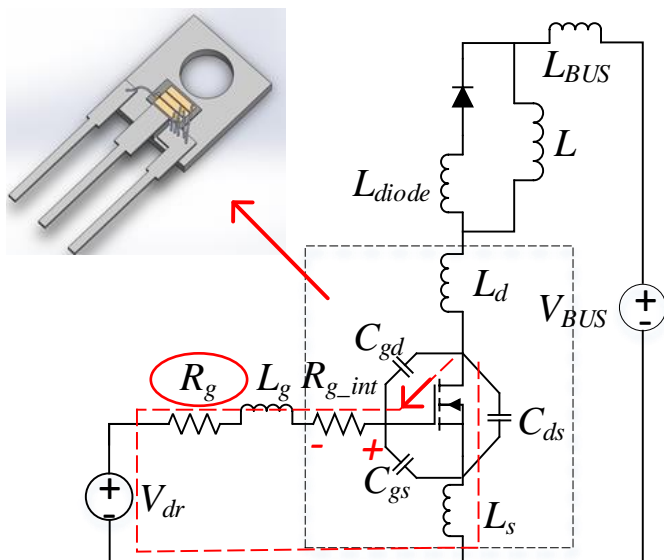
# Active Current Sharing Methodologies

How can we adjust static current distribution? – Adjustable  $V_{gs}$

How can we adjust the switching transient? – Maybe  $R_g$ ?




□ The equivalent circuit of a power MOSFET

$C_{gd}$ : Miller capacitor

$C_{gs}$ : gate-source capacitor

$L_s, L_d$ : parasitic stray inductance

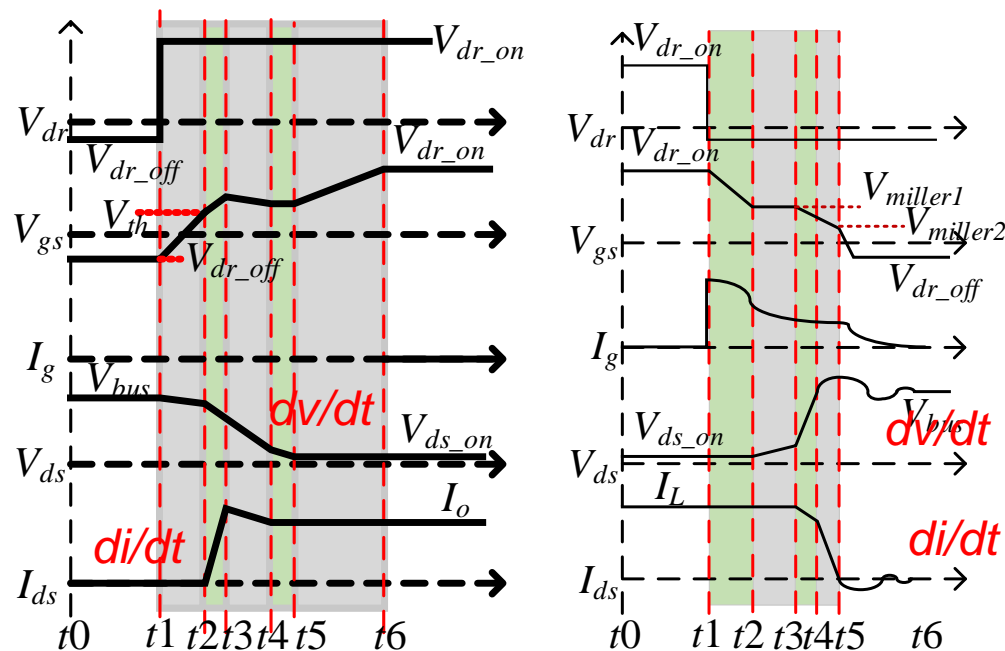

Normal turn-on


Normal turn-off

- ❖ Fast switching -> Lower losses -> High EMI noise
- ❖ Switching speed cannot be adjusted actively
- ❖ Adjusting the switching speed through changing  $R_g$

# Active Current Sharing Methodologies

## What parameters impact the switching transient? – Trajectory model tells you
 
### □ Trajectory Model Introduction: Turn-off Delay Stage ( $t_1 \sim t_3$ )




- Target: reduce the turn-off delay

$$\text{Duration } t_{delay} = R_g (C_{gs} + C_{gd}) \ln\left(\frac{V_{dr\_on} - V_{dr\_off}}{V_{miller1} - V_{dr\_off}}\right)$$

$$\text{where } V_{miller1} = \frac{I_o}{g_{fs}} + V_{th}$$

$V_{miller1}$ : Miller plateau voltage

 


Conclusion:

- ✓ Turn-off delay is related with  $V_{int}$ , but not with  $I_o$
- ✓ Power losses and EMI is almost zero in this period

# Active Current Sharing Methodologies
 
## □ Trajectory Model Introduction: Voltage Rising Stage ( $t_3 \sim t_4$ )




- Target: reduce the  $dv/dt$
- Must consider the non-linear  $C_{gd}$


$$C_{gd} \text{ vs. } V_{ds} \quad C_{gd} = \frac{C_{gd0}}{\sqrt{1 + V_{ds} / \phi_0}}$$

$$\frac{dv}{dt} = \frac{V_{BUS}}{t_{VR}} = \frac{V_{BUS} (V_{miller1} - V_{int})}{4C_{gd0} R_g \phi_0 (\sqrt{1 + V_{BUS} / \phi_0} - 1)}$$
 
$$\text{Energy loss } E_{VR} = \int_{t=0}^{t_{VR}} V_{ds} I_{ds} dt = \frac{dv}{dt} \frac{(2I_{ds4} + I_o) t_{VR}^2}{6}$$



$dv/dt$  vs. load current and  $V_{int}$

 


Energy losses vs. load current and  $V_{int}$

- ✓ High  $V_{int} \rightarrow$  Low  $dv/dt \rightarrow$  High power losses
- ✓ The  $dv/dt$  and power losses are all HIGH during this period

# Active Current Sharing Methodologies
 
## □ Trajectory Model Introduction: Current Falling Stage ( $t_4 \sim t_5$ )




- Target: reduce the  $di/dt$  and voltage overshoot
- Non-saturation condition:  $V_{int} < V_{th}$


$$di/dt \quad di/dt = \frac{I_{ds4}}{t_{CF1}} = \frac{g_{fs} (0.5V_{th} + 0.5V_{miller2} - V_{int})}{R_g C_{iss} + L_s g_{fs}}$$

Energy loss:
 
$$E_{CF} = \frac{t_{CF1} V_{BUS} I_{ds4}}{2} = \left[ I_o - (C_d + C_L) \frac{I_o + (V_{th} - V_{int}) g_{fs}}{2R_g C_{gd} g_{fs}} \right] \frac{(R_g I_{ds4} C_{iss} + L_s g_{fs} I_{ds4}) V_{BUS}}{g_{fs} (V_{th} - V_{int})}$$



 The  $di/dt$  vs. load current and  $V_{int}$




The energy losses  $E_{CF}$  vs. load current and  $V_{int}$

- ✓ High  $V_{int} \rightarrow$  Low  $di/dt \rightarrow$  High power losses
- ✓ The  $di/dt$  and power losses are all HIGH during this period



# Active Current Sharing Methodologies
 
## □ Trajectory Model Introduction: Current Falling Stage ( $t_4 \sim t_6$ )




- Target: reduce the  $di/dt$  and voltage overshoot
- Saturation condition:  $V_{int} > V_{th}$ , the  $V_{int}$  is not able to completely shut down the device


$$\text{Saturation current } I_{sat} = \frac{k_p}{2} (V_{int} - V_{th})^2$$

$$di/dt_{-I} = \frac{I_o - (C_d + C_L)(V_{BUS} - V_{miller1} + V_d + V_{th}) / t_{VR} - I_{sat}}{t_{CF2}}$$
 
$$di/dt_{-II} = \frac{I_{sat}}{t_V} = \frac{I_{sat}}{(C_{gd} + C_{gs})R_g \ln\left(\frac{V_{int} - V_{dr\_off}}{V_{th} - V_{dr\_off}}\right)}$$



 The  $di/dt$  vs. load current and  $V_{int}$



The energy losses  $E_{CF}$  vs. load current and  $V_{int}$

✓ High  $V_{int} \rightarrow$  Low  $di/dt_{-I} \rightarrow$  High  $di/dt_{-II} \rightarrow$  High power losses

✓ The  $di/dt$  and power losses are all HIGH during this period


# Active Current Sharing Methodologies

## Conclusions: How can we implement switching process control?

❑ Five freedoms:  $R_g$ ,  $C_{iss}$ ,  $I_g$ ,  $V_{dr}$ , and time delay






❑ Five State-of-the-Art AGD Methodologies

- Change  $R_g$ : Variable gate resistance method
- Easy to implement, low resolution
- Change  $C_{iss}$ : Variable input capacitance method
- Hard to change capacitance actively
- Change  $I_g$ : Variable gate current method
- Good oscillation suppression, remove  $R_g$
- Hard to design
- Change  $V_{dr}$ : Variable gate voltage method
- Easy to implement DESAT protection
- High resolution, easy adjustment
- Change  $delay$ : Variable delay time method
- Easy to implement DESAT protection
- High resolution, easy adjustment

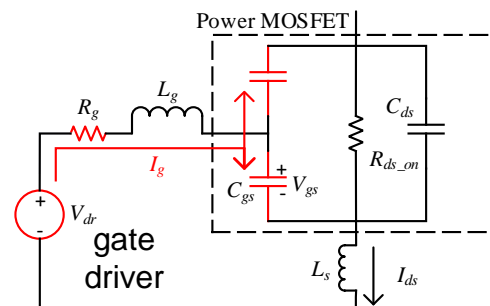


Turn on  
 $V_{gs} > V_{th}$

Turn off  
 $V_{gs} < V_{th}$

 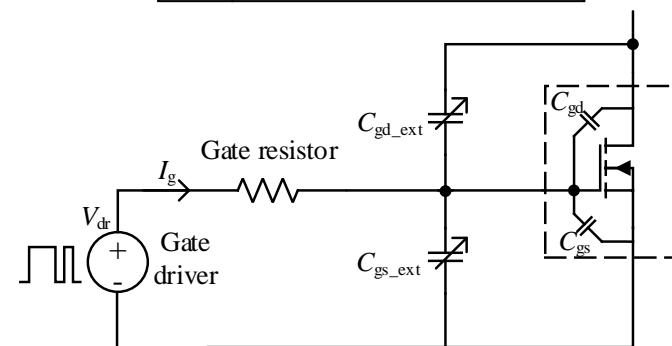   


# Active Current Sharing Methodologies

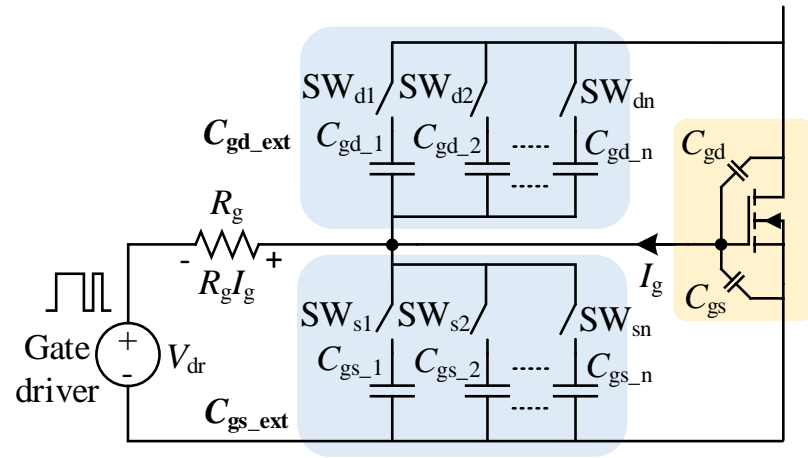
## What SOTA AGD circuitries do we have now?




Variable gate capacitance

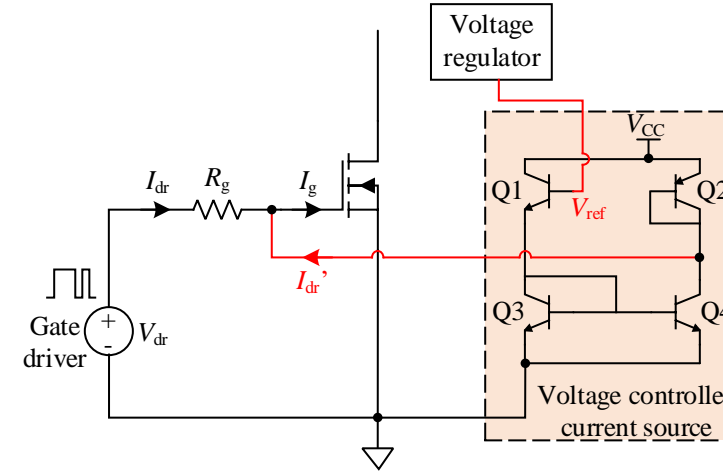

Variable gate current (Sun, VT, 2019)

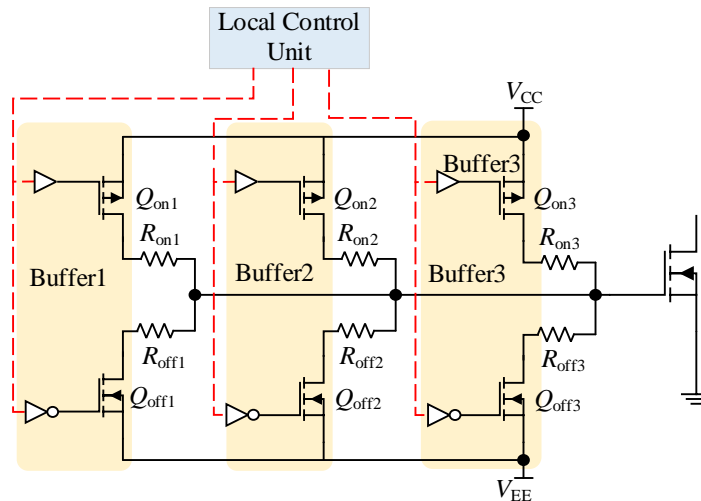

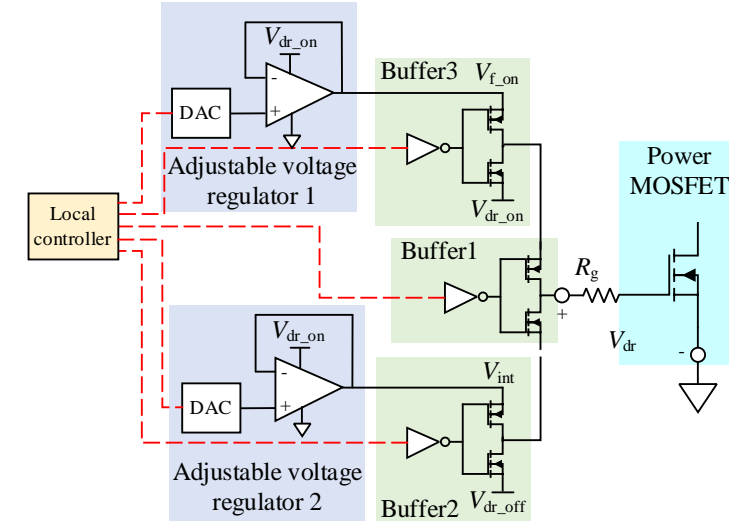Variable gate resistance (Engelmann, RWTH Aachen, 2019)




Variable gate voltage (Zhao, UArk, 2020)

[1] G. Engelmann, T. Senoner and R. W. DeDoncker, "Experimental investigation on the transient switching behavior of SiC MOSFETs using a stage-wise gate driver," *CPSS Trans. Power Electron. Appl.*, vol. 3, no. 1, pp. 77-88, 2018.

[2] Sun, R. Burgos, X. Zhang and D. Boroyevich, "Active dv/dt control of 600V GaN transistors," in Proc. Energy Conv. Congr. Expo., Milwaukee, WI, USA, 2016.

# Active Current Sharing Methodologies
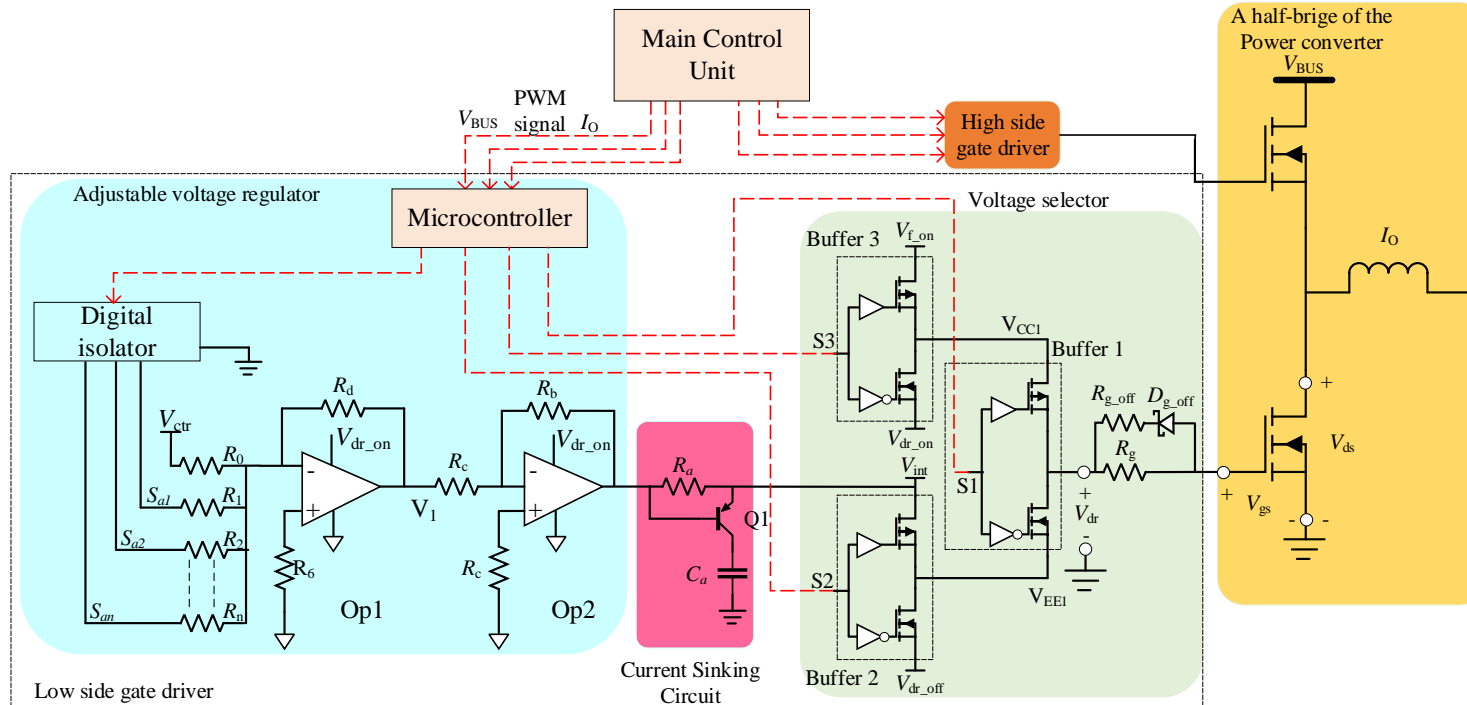
## How can we implement a true AGD? – An example



- Microcontroller: Control the AGD and conduct optimization


- Adjustable voltage regulator: generate the intermediate voltage level

- Current sinking circuit: Assist in sinking reversed flowing gate current

- Voltage selector: generate the multi-level driver voltage profile

# Active Current Sharing Methodologies

## □ The active voltage regulator

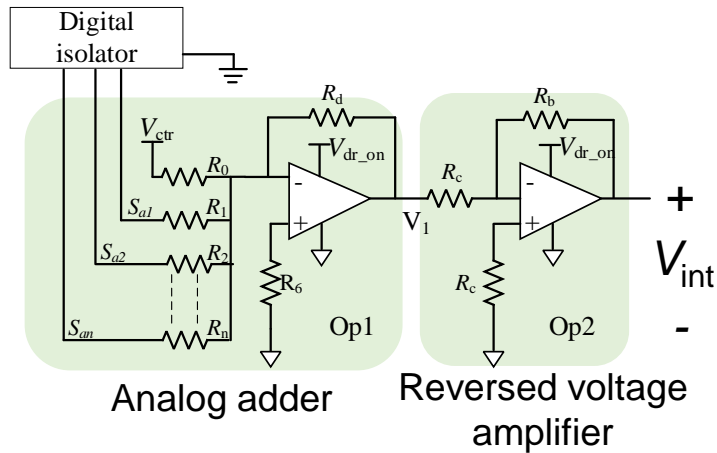

Output of voltage regulator

$$V_{int} = V_{ctr} \left( \frac{1}{R_0} + \frac{S_{a1}}{R_1} + \frac{S_{a2}}{R_2} \dots \frac{S_{an}}{R_n} \right) R_d \frac{R_b}{R_c}$$

Herein,  $S_{a1} - S_{an} = 0$  or  $1$


Relationship of the resistors

$$R_1 = 2^1 R_2 = 2^2 R_3 = 2^{n-1} R_n$$

## □ The current sinking circuit


The design criterion:

$$I_g R_a \geq V_{BE\_on}$$

 

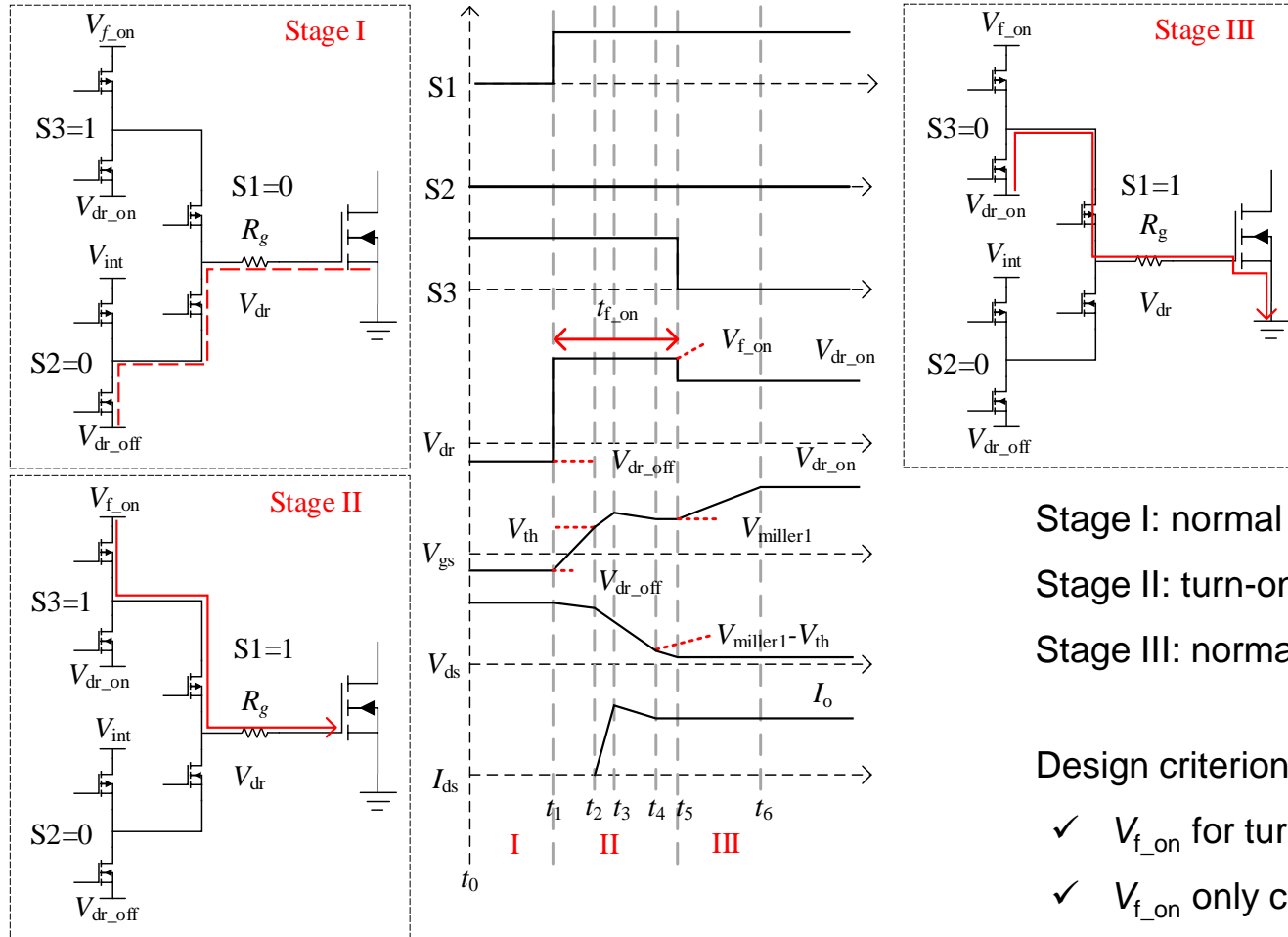
# Active Current Sharing Methodologies

□ The working principle of voltage selector: Faster turn-on



# Active Current Sharing Methodologies

□ The working principle of voltage selector: Slower turn-on

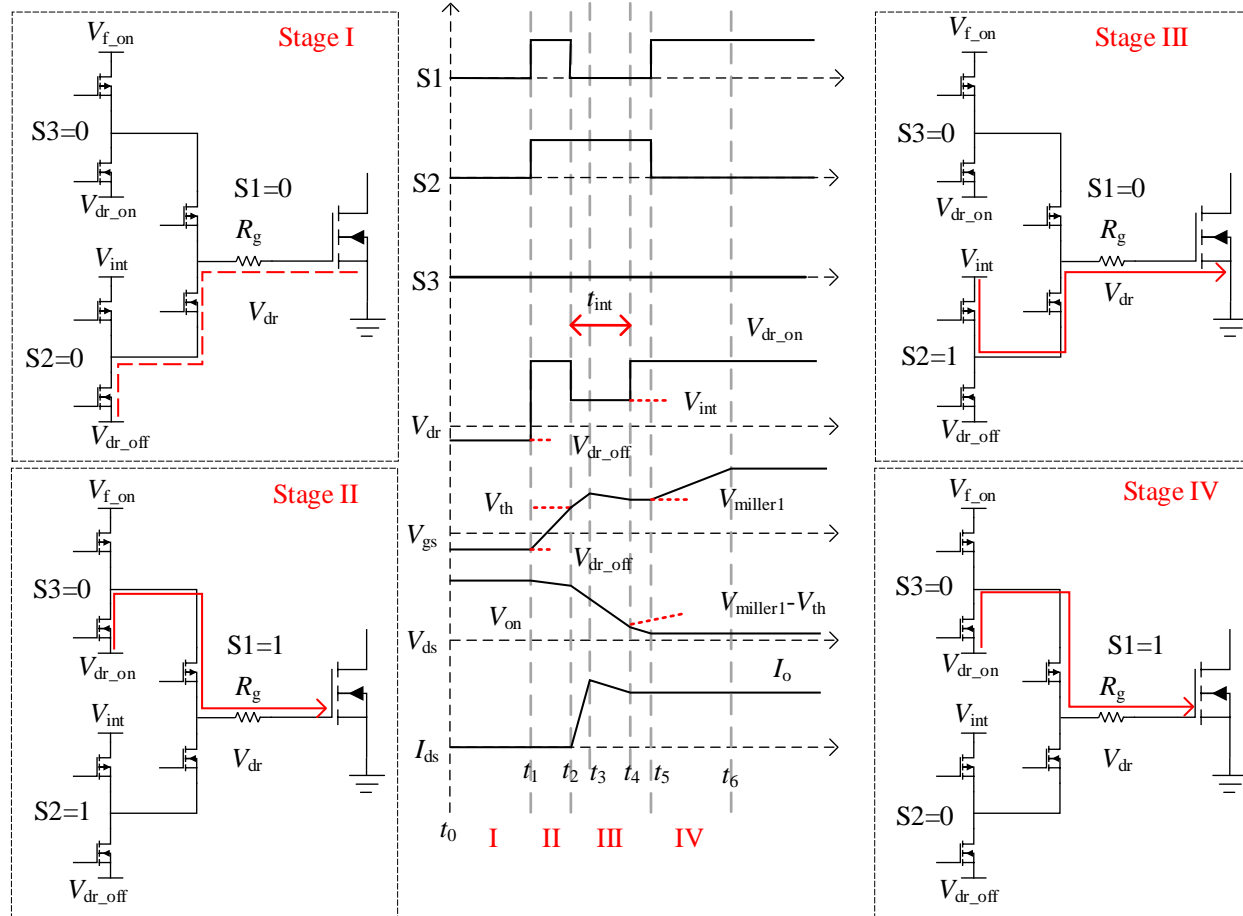

Stage I: normal turn-off

Stage II: turn-on delay

Stage III: Miller plateau


Stage IV: normal turn-on

Design criterion:

- ✓  $V_{dr\_on}$  for shortening turn-on delay
- ✓  $V_{int}$  only covers voltage falling time and current rising time
- ✓  $V_{dr\_on}$  for normal turn-on condition

# Active Current Sharing Methodologies

□ The working principle of voltage selector: Slower turn-off

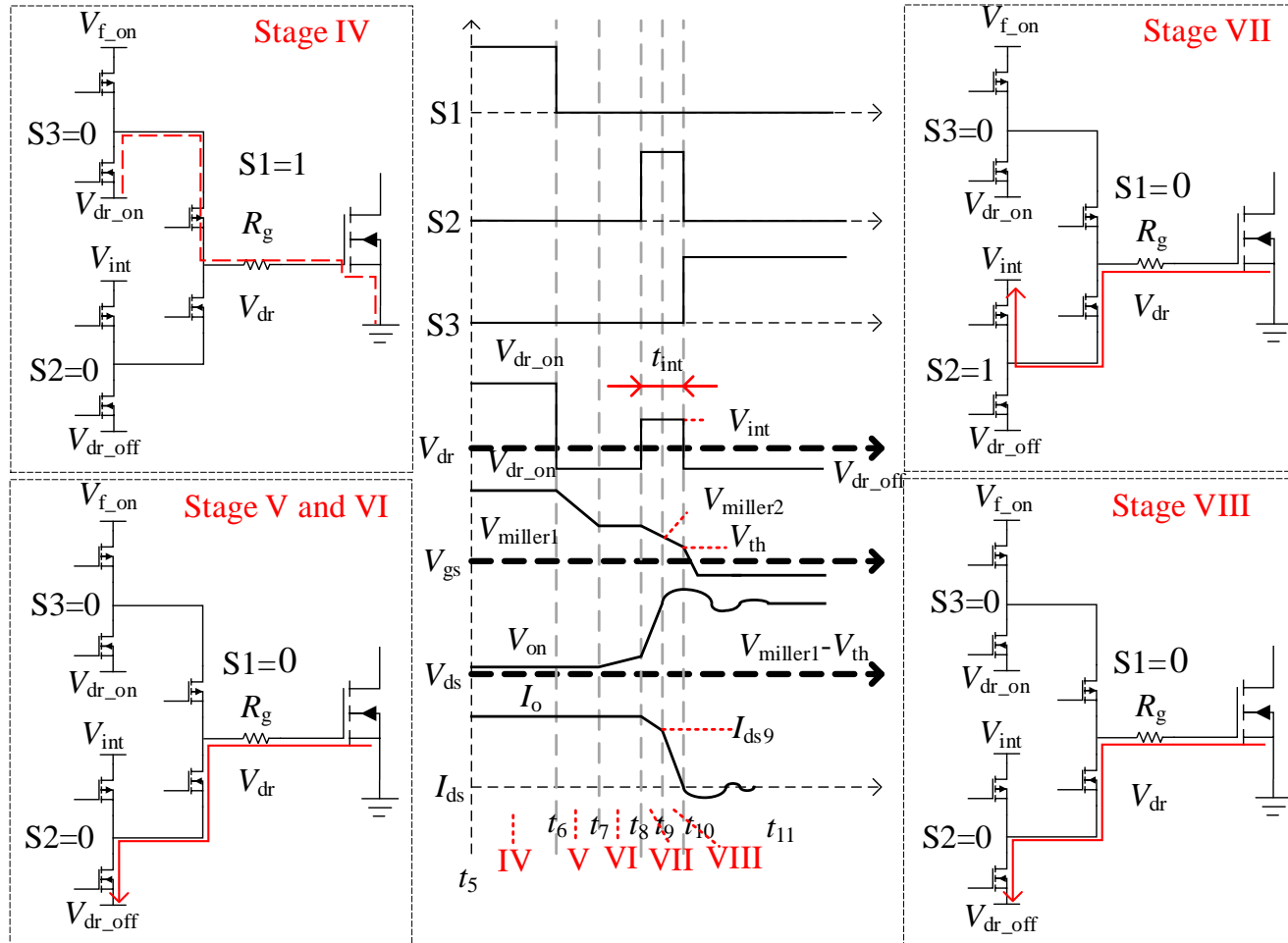

Stage IV: normal turn-on

Stage V: turn-off delay

Stage VII: Miller plateau

Stage VIII: normal turn-off

Design criterion:

- ✓  $V_{dr\_off}$  for shortening turn-off delay
- ✓  $V_{int}$  only covers voltage rising time and current falling time
- ✓  $V_{dr\_off}$  for normal turn-off condition



# Active Current Sharing Methodologies

## How can we capture the true switching waveform of WBG? – Measurement matters!

### ❑ Measurement for SiC power MOSFET

- ✓ Shorten the measurement loop: reduce measurement EMI



$V_{ds}$  measure: Use BNC adaptor



$V_{gs}$  measure: Use MMCX connector OR optical isolated probe (very expensive)



Use wire wound connection instead of alligator clip

- ✓ Current measurement




T&M coaxial shunt



Paralleling SMD resistor shunt + MMCX
 
### Shunt resistor:

- ✓ High bandwidth:  $\geq 400$  MHz
- ❖ Carefully design the grounding




### Rogowski coil


- ✓ Isolation
- ❖ Lower bandwidth: 30 MHz
 
# Active Current Sharing Methodologies

- ❑ Designed gate driver – For 1.2 kV SiC power MOSFET



 
1.2 kV intelligent active gate driver setup



Active gate driver board Ver. 5

- Active gate driver
- ✓ 64 levels of  $V_{int}$  adjustment
- ✓ Very fast speed: 3.3 ns
- ✓ 2.5 kV isolation levels

CREE conventional gate driver

 


Active gate driver for 1.2 kV/300A half-bridge SiC


- Active gate driver
- ✓ Compatible with CREE gate driver
- ✓ DESAT Protection
- ✓ Junction temperature

# Active Current Sharing Methodologies

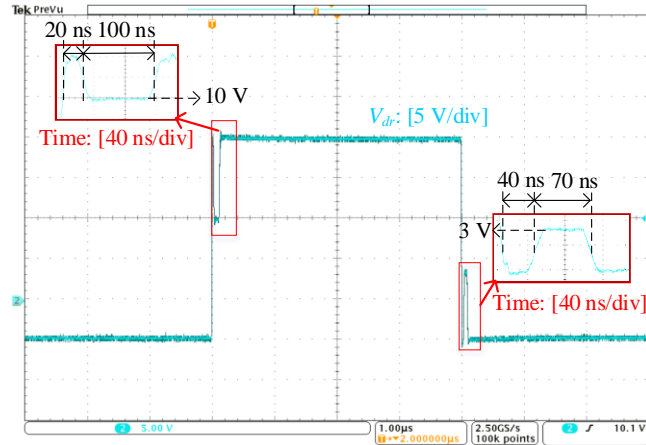
## ❑ Empty load experiments results of the AGD




Slower turn-on and slower turn-off

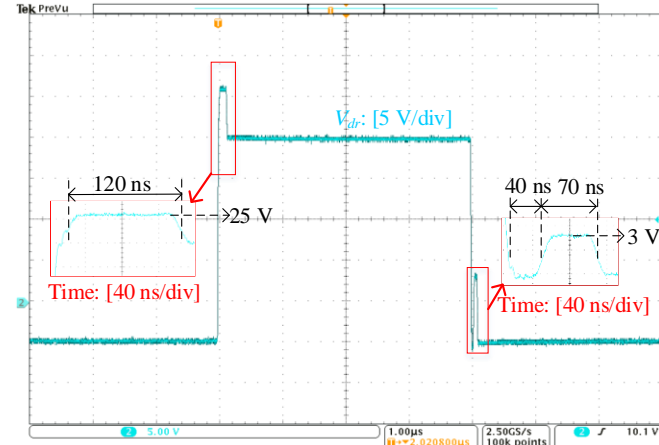

Faster turn-on and slower turn-off

 




Normal turn-on and normal turn-off

 

$V_{int}$  and duration are adjustable

# Active Current Sharing Methodologies
   
## Experimental verification on 1.2 kV devices



### □ Faster turn-on mode

- ✓ Reduce turn-on losses (770  $\mu J$  -> 660  $\mu J$ , 17%)
- ✓ Increases turn-on current overshoot (40%-> 57%)

### □ Slower turn-on mode

- ✓ Increase turn-on losses
- ✓ Reduce turn-on current overshoot

### □ Slower turn-off mode


- ✓ Increase turn-off losses
- ✓ Reduce turn-off voltage overshoot





# Active Current Sharing Methodologies

## What fancier stuff can we make? – AGD for 10 kV SiC MOSFET
 
### ❑ Designed PCB – For 10 kV SiC MOSFET





Active gate driver for 10 kV module

  



- Online adjustment
- Adaptive control for the slew rate
- Same performance in control and circuitry with 1.2 kV version
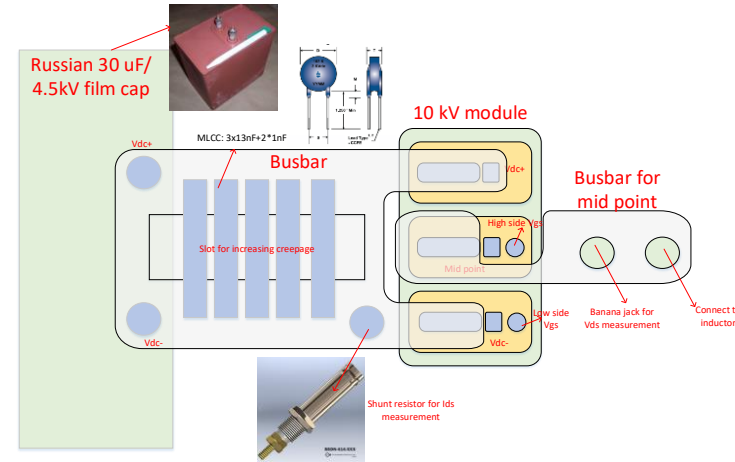 
# Active Current Sharing Methodologies

- ❑ Designed bus bar – For 10 kV SiC power MOSFET




 
 
- ❑ DSP controller with the fiber transmitter



10 kV double pulse test setup

# Active Current Sharing Methodologies
   
## Experimental verification on 10 kV devices



### Comparison of slower turn-off with different $V_{int}$

$V_{int}$	$dv/dt$ (V/ns)
Conventional	94.78
5 V	58.8
5.6 V	54.32
6.3 V	52.4
6.9 V	49.16
7.5 V	43.56
8.1 V	40.37

### Comparison of slower turn-off with different $I_{ds}$ , ( $V_{int} = 7.2$ V)


$V_{int}$	Energy losses
Conventional	2302 $\mu J$
5 V	4384 $\mu J$
5.6 V	4629 $\mu J$
6.3 V	4977 $\mu J$
6.9 V	5555 $\mu J$
7.5 V	6259 $\mu J$
8.1 V	7410 $\mu J$

### Comparison of CGD with AGD


$V_{int}$	$di/dt$ (A/ns)
Conventional	0.34
5 V	0.158
5.6 V	0.145
6.3 V	0.138
6.9 V	0.122
7.5 V	0.109
8.1 V	0.097
 
# Active Current Sharing Methodologies


Does that work on current sharing? – Try!




ANSYS-assisted layout design

 

 Adjustable gate driver: delay time + driver voltage



Tek 500MHz 8-channels oscscope

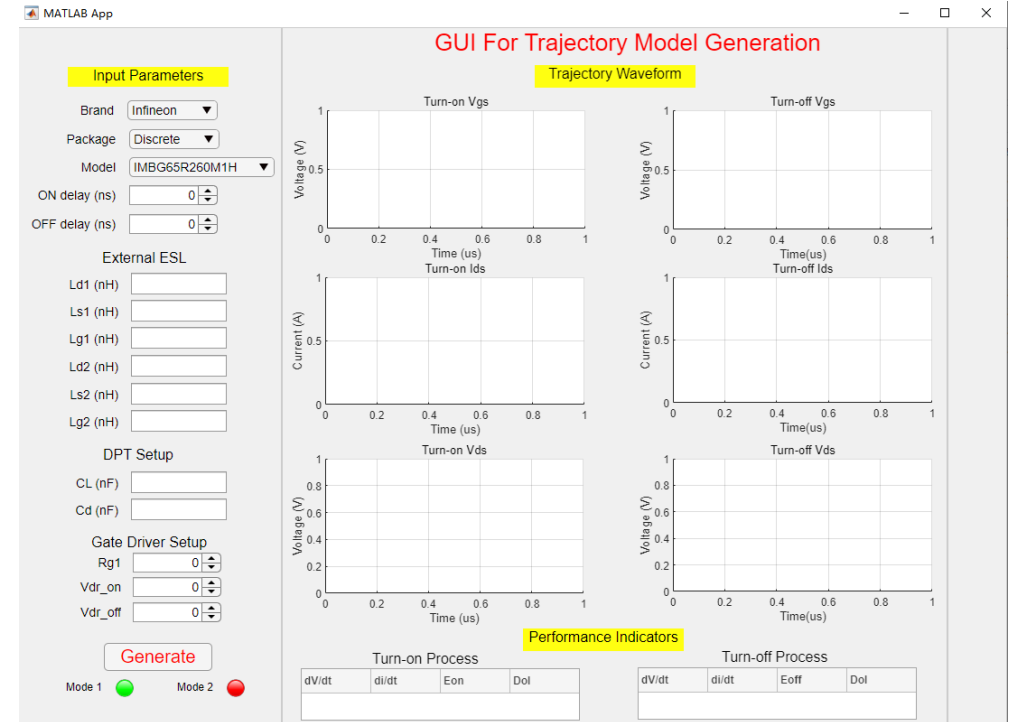


GUI for paralleling MOSFET modeling





 
# Active Current Sharing Methodologies


□ With adjustable delay time gate driver for transient balance




Turn-on process

 

 Turn-on process: adjustable turn-on delay





Turn-off process


 


Turn-off process: adjustable turn-on delay

  □ With adjustable  $V_{dr}$  for transient balance



Turn-on process without AGD

  

Turn-on process with AGD

# Part II – Active Current Sharing Methodologies

03

● Conclusions and insight ●

# Conclusions and Insight



## ❑ Conclusions

Current sharing solutions



- Power module:
  - preselection of chips
  - optimization of package layout
  - Optimization of PCB/bus bar layout
- External passives:
  - L/C/R
  - Hybrid
- Driver-based:
  - Static – Only change  $V_{dr}$
  - Five adjustable freedoms



## ❑ Insight

Challenges for external passives:


- ❑ Higher cost -> Commercialization
- ❑ Longer power loop can increase the parasitics
- ❑ Higher impedance can reduce the system efficiency

Challenges for AGD-based:

- ❑ Higher cost and complicated circuitry -> Struggling for **commercialization**
- ❑ Very fast switching transient of SiC -> Difficult for **Feedback** control and timing sequence design

Optimization of the power device/module:

 - ❑ Preselection of chips + circuit layout optimization: Still the most preferred solution in the industry
- ❑ Automatic layout generation tools needed in the future



Microchip AgileSwitch AGD

- [1] H. Li, S. Munk-Nielsen, X. Wang, R. Maheshwari, S. Beczkowski, C. Uhrenfeldt, W.-Toke Frank, 'Influences of Device and Circuit Mismatches on Paralleling Silicon Carbide MOSFETs', IEEE Transaction on Power Electronics, Vol.31, No.1, pp:621 - 634, Jan.2016.
- [2] H. Li, S. Munk-Nielsen, S. Beczkowski, X. Wang, 'A novel DBC layout for current imbalance mitigation in SiC MOSFET multichip power modules', IEEE Transaction on Power Electronics, vol. 31, no. 12, pp. 8042-8045, Dec.2016.
- [3] H. Li, S. Munk-Nielsen, X. Wang, S. Beczkowski, S. Jones, X. Dai, 'Effects of Auxiliary-Source Connection in Multichip Power Modules', IEEE Transaction on Power Electronics, Vol.32, No.10, pp:7816 - 7823, Oct.2017.
- [4] H. Li, W. Zhou, X. Wang, S. Munk-Nielsen, D. Li, Y. Wang, X. Dai, 'Influence of Paralleling dies and Paralleling Half Bridges on Transient Current Distribution in Multichip Power Modules' IEEE Transaction on Power Electronics, Vol.33, No.8, pp:6483 - 6487, Aug.2018.
- [5] H. Li and S. Munk-Nielsen, "Challenges in Switching SiC MOSFET without Ringing," PCIM Europe, 2014, pp. 1-6.
- [6] H. Li, C. Zhu, P. Mumby-Croft, D. Li, Y. Wang and X. Dai, "Influence of Auxiliary Gate and Emitter Connections on Short Circuit Behaviour of Multichip IGBT Modules," PCIM Europe, 2018, pp. 1-5.
- [7] H. Li, S. Munk-Nielsen, C. Pham and S. Bęczkowski, "Circuit mismatch influence on performance of paralleling silicon carbide MOSFETs," 2014 16th European Conference on Power Electronics and Applications, 2014, pp. 1-8.
- [8] Helong Li and S. Munk-Nielsen, "Detail study of SiC MOSFET switching characteristics," 2014 IEEE 5th International Symposium on Power Electronics for Distributed Generation Systems (PEDG), 2014, pp. 1-5.
- [9] N. Baker, F. Iannuzzo and H. Li, "Impact of Kelvin-Source Resistors on Current Sharing and Failure Detection in Multichip Power Modules," *2018 20th European Conference on Power Electronics and Applications (EPE'18 ECCE Europe)*, 2018, pp. 1-7.
- [10] H. Li, S. Beczkowski, S. Munk-Nielsen, R. Maheshwari and T. Franke, "Circuit mismatch and current coupling effect influence on paralleling SiC MOSFETs in multichip power modules," *Proceedings of PCIM Europe*, 2015, pp. 1-8.



- [11] S. Zhao, X. Zhao, A. Dearien, Y. Wu, Y. Zhao, and H. A. Mantooth, "An intelligent versatile active gate driver for high-voltage SiC MOSFET and its optimization," *IEEE J. Emer. Sel. Topics Power Electron.*, vol. 8, no. 1, pp. 429-441, Jun. 2020
- [12] S. Zhao *et al.*, "Adaptive multi-level active gate drivers for SiC power devices," *IEEE Transaction on Power Electronics.*, vol. 35, no. 2, pp. 1882-1898, Feb 2020.
- [13] S. Zhao, X. Zhao, Y. Wei, Y. Zhao and H. A. Mantooth, "A review on switching slew rate control for silicon carbide devices using active gate drivers," *IEEE J. Emerg. Sel. Topics Power Electron.*, vol. 9, no. 4, pp. 4096-4114, Jul. 2020.
- [14] S. Zhao, A. Kempitiya, W. T. Chou, V. Palija and C. Bonfiglio, "Variable dc-link voltage LLC resonant DC/DC converter with wide bandgap power devices," *IEEE Transactions on Industry Applications*, vol. 58, no. 3, pp. 2965-2977, Feb. 2022.
- [15] A. Dearien, S. Zhao, C. Farnell, and H. A. Mantooth, "Active slew rate control for SiC power MOSFETs using gate resistance vs. intermediate voltage level," in Proc. Int. Conf. Power. Electron.(ICPE-ECCE Asia), Busan, Korea, 2019.
- [16] S. Zhao, H. A. Mantooth, A. Dearien, An intelligent multi-level active gate driver for SiC power MOSFET, US11277127B1, Feb. 2022
- [17] S. Zhao and W. Chou, "Analytic Model of the Voltage Oscillation in a Power Conversion System with DC-Link Capacitors," 2021 IEEE Energy Conversion Congress and Exposition (ECCE), 2021, pp. 5554-5560.
- [18] S. Zhao, M. Zhang, H. Li, A kind of SiC MOSFET switching waveform regaining method based on the switching trajectory model (Pending China Patent, 2022)
- [19] S. Zhao, C. Wang, H. Li, L. Ding, A kind of current measurement system for paralleling SiC MOSFET current, (Pending China Patent, 2022)
- [20] M. Zhang, S. Zhao, H. Li, L. Ding, Trajectory-Model-Based Switching Waveform Restoration Method for Accurate Dynamic Characterization of SiC Power MOSFET, in Proc. PEAC, Guangzhou, China, 2022 (Accepted)
- [21] C. Wang, S. Zhao, L. Ding, Analytical Model of the Parallel-Connected Silicon Carbide MOSFET Switching Behavior Under Asynchronous Gate Signals, in Proc. ITEC-AP, Haining, Zhejiang, China, 2022 (Accepted)

---

# Parallel-Connected SiC MOSFETs – Essence, Challenges, and Solutions

**Thanks!**

shuang.zhao@hfut.edu.cn

shuang.zhao@ieee.org